

---

# CS 2110 - Lab 05

State Machines & the LC-3

Monday, June 6th, 2021





## Lab Assignment: LC3 Quiz!

- 1) Go to Quizzes on Canvas
- 2) Select Lab 05, password: **Bus**
- 3) Get a 100% to get attendance!
  - a) Unlimited attempts
  - b) Collaboration is **allowed!**
  - c) Ask your TAs for help :)



## Homework 2

- Released!
- Due Monday, June 6<sup>th</sup> (today!) at 11:59 PM
- Files available on Canvas
- Submit on Gradescope
  - Double check that your grade on Gradescope is your desired grade!



## Homework 3

- Released!
- **Due Monday, June 13<sup>th</sup> at 11:59 PM**
- Files available on Canvas
- Submit on Gradescope (unlimited submissions)



## Timed Lab 1

- Scheduled this Wednesday, June 8<sup>th</sup> (next lab!)
- 75 minutes to complete at the beginning of lab, then lab will be resumed.
- Will cover HW2 Material primarily
  - Please have Docker working on the device you bring to Lab! If you have any trouble, please see a TA ASAP
  - If you need outlet priority, please let a TA know ASAP
  - You may use any submitted homework files during the timed lab
  - Unlimited submissions throughout the TL period.



## Quiz 2

- **Next Wednesday, June 15<sup>th</sup>**
- Quiz opens at your assigned lab time (unless you have already established a different time with your professor)
- Full 75 minutes to take the quiz!
- After the quiz, you will join lab for the remaining period.
- A topic list will be posted on Canvas



# Today's Topics

- State Machines
  - One Hot
  - Binary Reduced
- The LC-3 Datapath
  - The Bus
  - Tri-state buffers
  - Control signals
  - Microcontrollers


# State Machines!

- Example: Dave, the Funky Dancing Robot Crab
  - Dave is a dancing robot crab. Before it can dance it must fully recharge (3 charges). It can recharge slow by solar energy (1 charge) or fast with a battery (2 charges).
  - Dave has 3 possible states:
    1. Dancing (requires 3 charges)
    2. Charging with 1 charge
    3. Charging with 2 charges







# Dave's State Transition Diagram

 
 
# State Transition Diagram - Representation




# State Machine Diagram - One Hot

 


# Truth Table - One Hot


P	$S_2S_1S_0$	$N_2N_1N_0$	L
X	000	001	0
0	001	010	0
1	001	100	0
0	010	100	1
1	010	001	1
0	100	001	1
1	100	001	1

 

# Circuit - One Hot

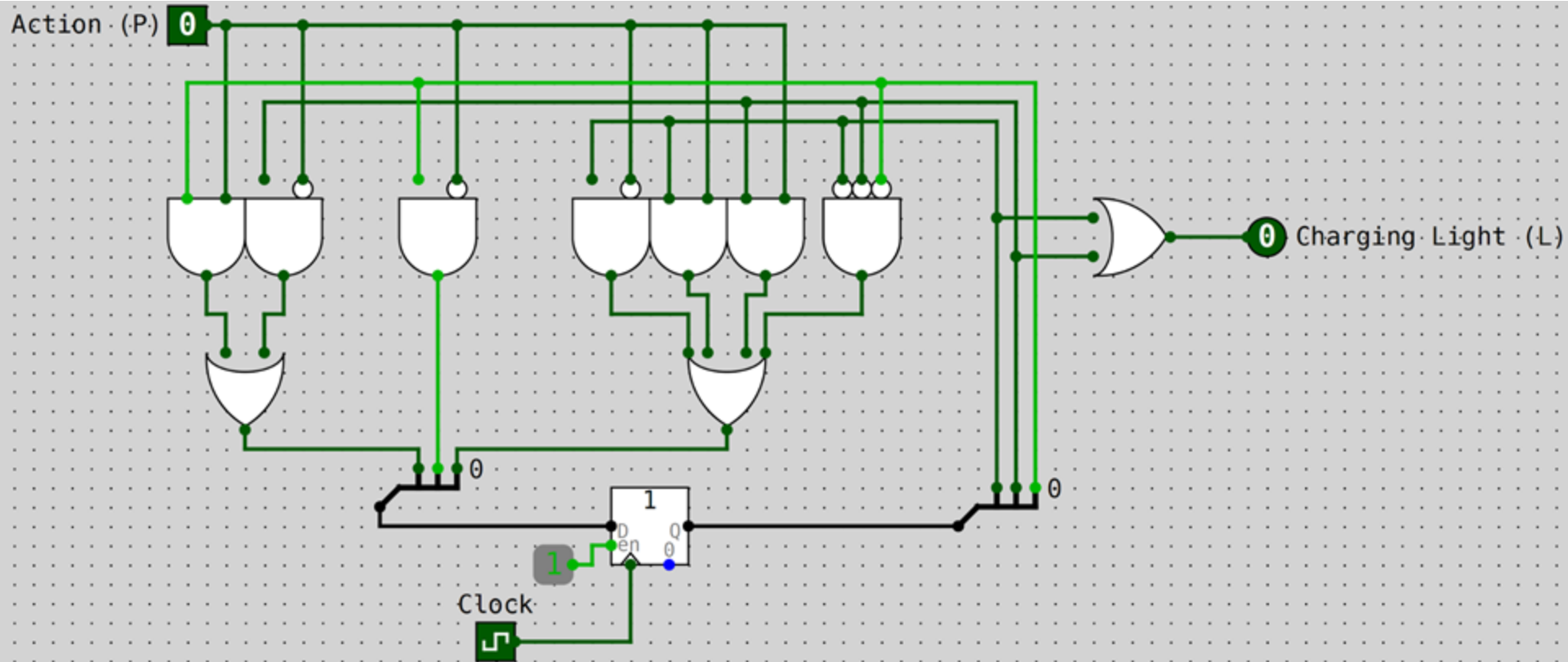

# State Machine Diagram - Binary Encoded

 

# Truth Table - Binary Encoded

P	$S_1S_0$	$N_1N_0$	L
0	00	01	0
1	00	10	0
0	01	10	1
1	01	00	1
0	10	00	1
1	10	00	1
0	11	XX	X
1	11	XX	X

Since we only have three inputs (P,  $S_1$ ,  $S_0$ ), we can use K-maps to create a simpler circuit. We have to create one K-map for each output.

$N_1$	$S'_1S'_0$	$S'_1S_0$	$S_1S_0$	$S_1S'_0$
$P'$	0	1	X	0
$P$	1	0	X	0

$$N_1 = S'_1S'_0P + S_0P'$$


$N_0$	$S'_1S'_0$	$S'_1S_0$	$S_1S_0$	$S_1S'_0$
$P'$	1	0	X	0
$P$	0	0	X	0

$$N_0 = S'_1S'_0P'$$

L	$S'_1S'_0$	$S'_1S_0$	$S_1S_0$	$S_1S'_0$
$P'$	0	1	X	1
$P$	0	1	X	1

$$L = S_0 + S_1$$

# Circuit - Binary Encoded

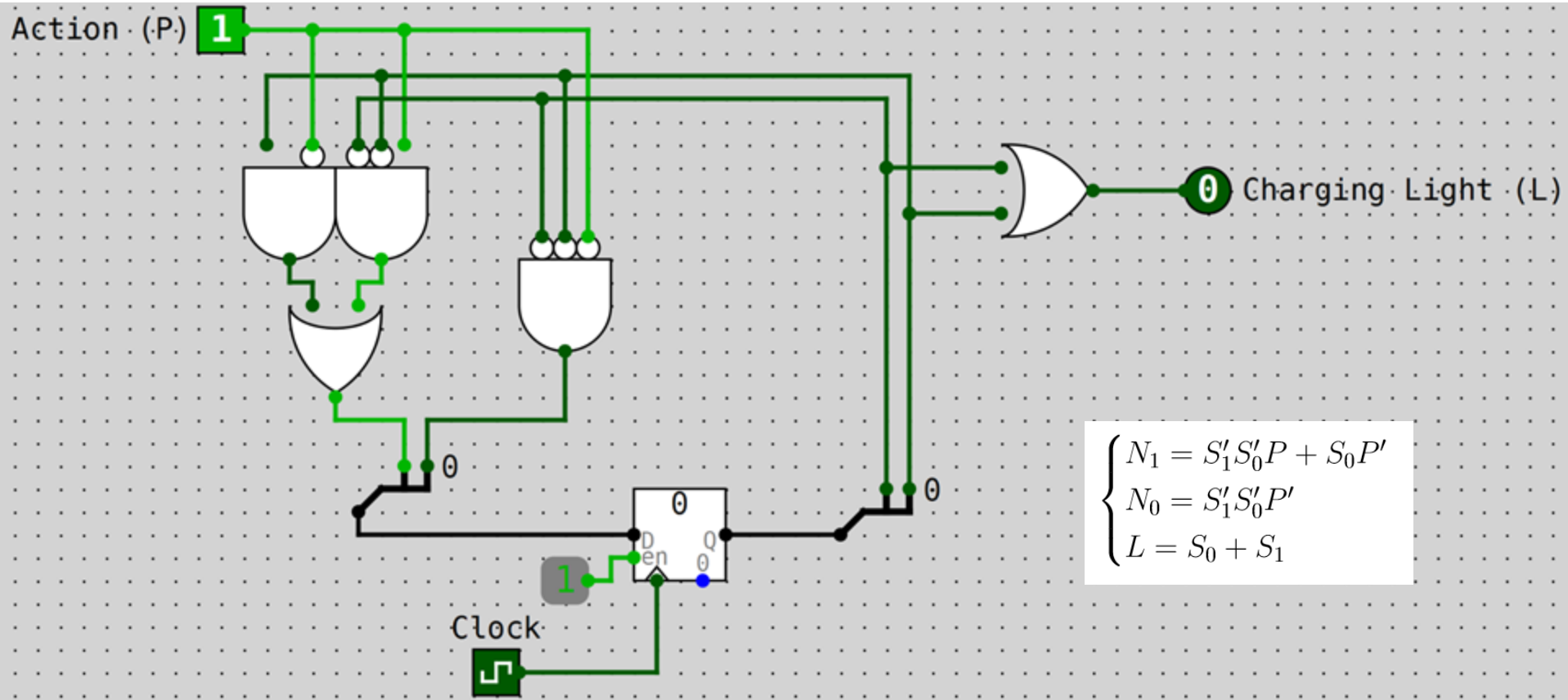






## A word of caution...

- State machines are NOT event-driven; they are locked to the clock
- The state is always updated once per clock cycle, even if you transition into the same state
- This is true of all sequential logic in modern computers




**Given a state machine with 20 states, how many bits do you need to represent it in a one-hot state machine?**



 **Given a state machine with 17 states, how many bits do you need to represent it in a binary encoded state machine?**

Which of the following is a correct boolean expression for  $N_3$ ?


- $S_0B' + S_1B + S_3'$
- $S_0B' + S_1B + S_2B$
- $S_1B + S_2B$
- $N_0B + N_1B' + S_0B'$





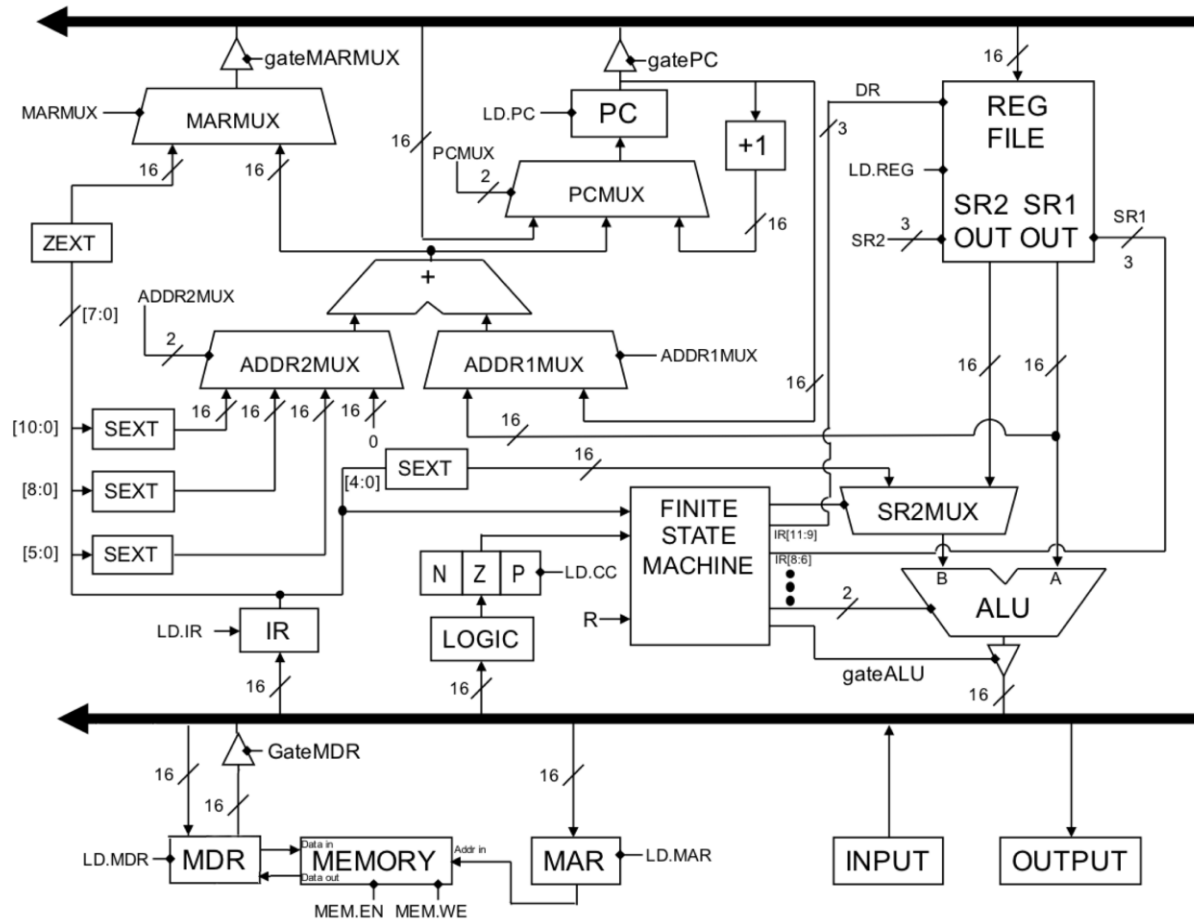
## Intro to the LC-3

- A pedagogical processor architecture
- Combines everything we've learned so far
  - ALU, state machine, registers, memory, etc.
- Looks intimidating, but we'll break it down into its components




# LC-3 Components

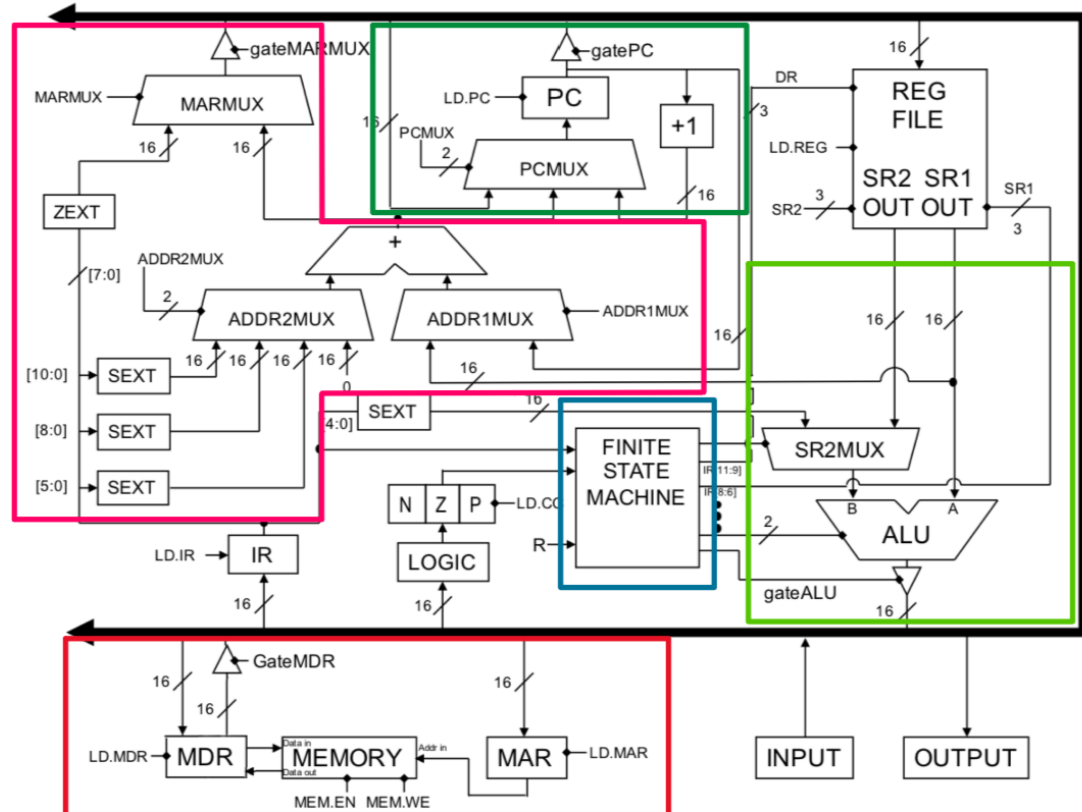
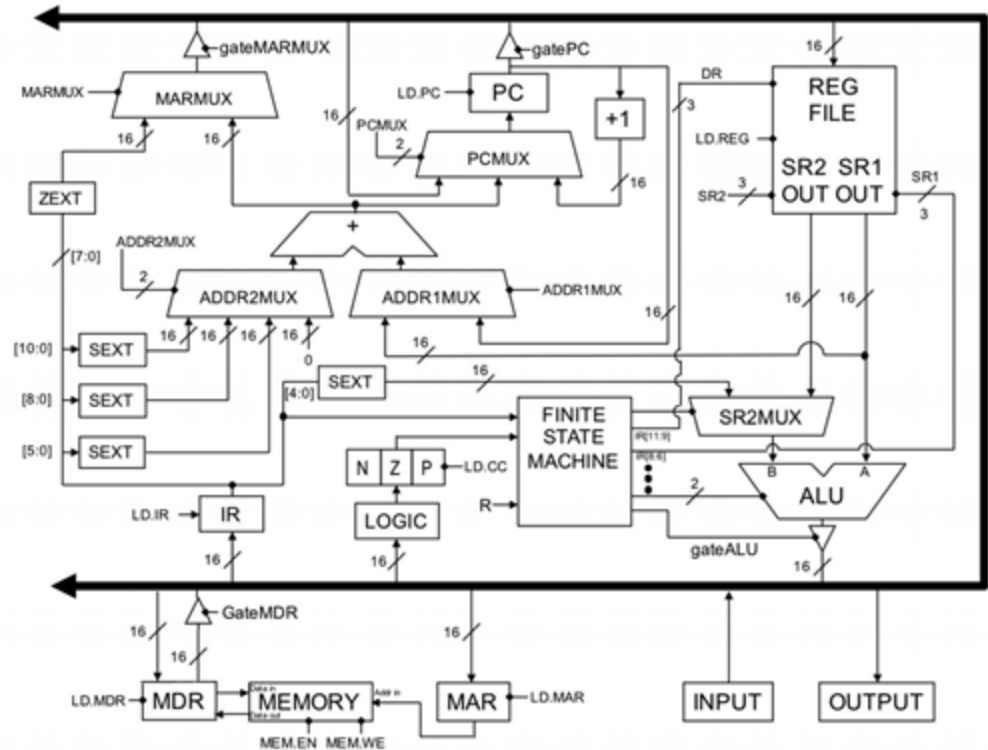
# The Bus



- 16-bit wire that transfers data between many components
- Only **one** value on wire at a time—why?




  
# Tristate Buffer


- Helps in making sure there is only one value on bus
- Driven through signals like GatePC, GateMDR, etc.



CONTROL	INPUT	OUTPUT
0	0	Z
0	1	Z
1	0	0
1	1	1

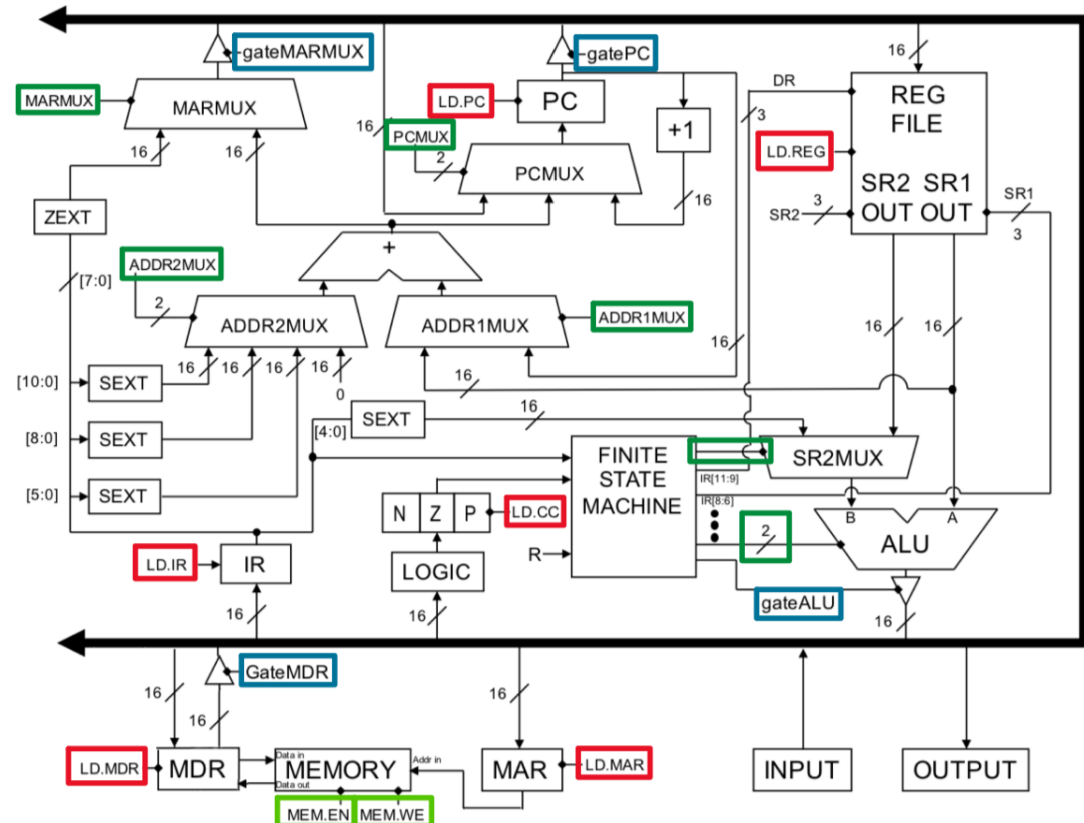
# Control Signals

- Used to move data around
  - LD.\_\_\_\_** – write enable for a register
  - gate\_\_\_\_** – tri-state buffer that allows data to go onto the bus
  - \_\_\_\_MUX** – selector for a multiplexer



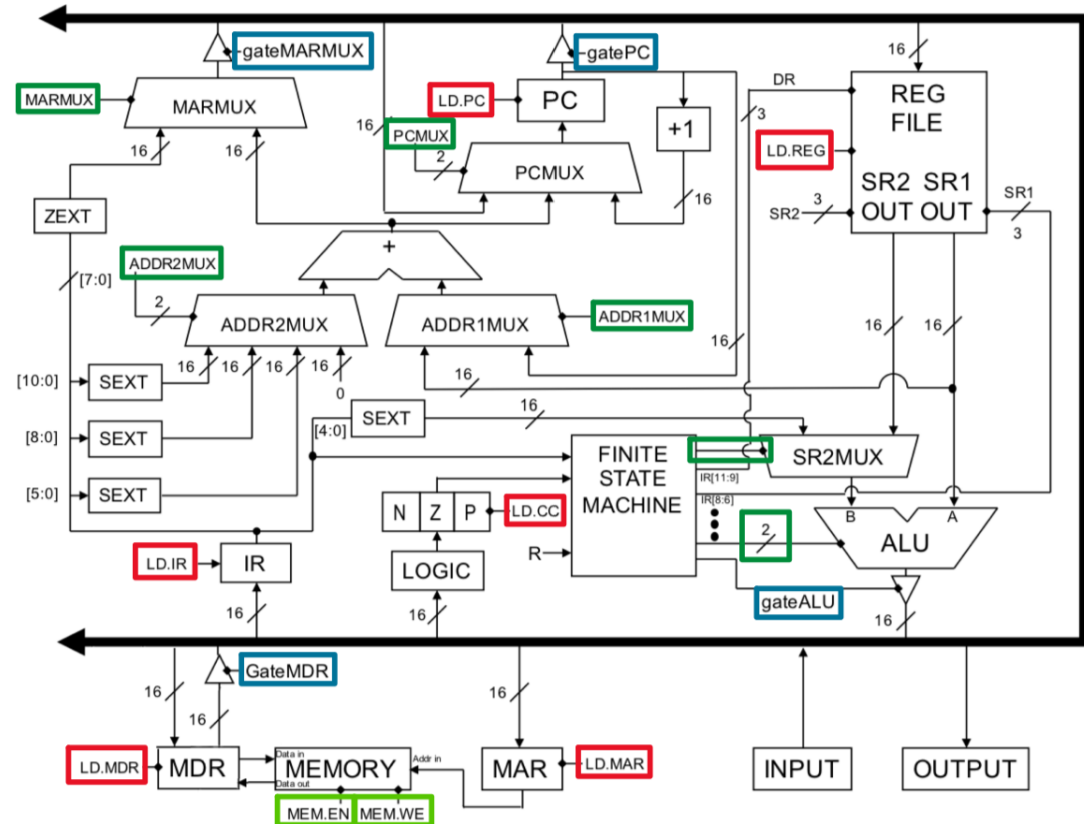
# Example

- Say we want to put the data from the PC (a register) into the MAR (another register). What signals do we turn on?





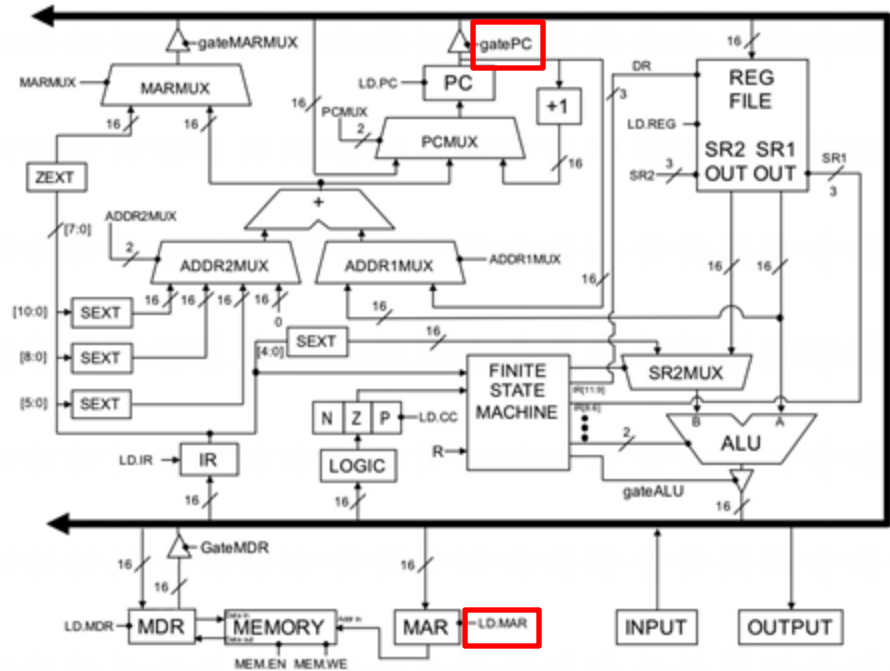




# Clock

- Clock cycles
  - Alternates between 0/1's
- One clock is connected to all the registers, keeping them in sync
- Ensure that we don't run into short circuits
- When a register has its Write Enable on, the next clock edge saves its current input

 
# The Microcontroller

- Finite state machine (FSM)
- Every instruction has a series of states to execute it
- Like in HW3, each state has
  - A set of outputs (control signals like ALUK, LdReg, etc.)
  - The next state to go to
- Ensures that correct operations take place, while preventing short circuits
- You'll be filling in parts of the state machine truth table for HW4


 
# The Purpose of the FSM

- Turn control signals on/off which are sent out to the rest of the datapath
- Move between microstates in order to fetch, decode, and execute instructions (more on this soon)







# What is Memory? - Registers VS. Memory (RAM)

You have been exposed to **sequential logic**. (i.e. registers)

**Registers:** Used for quick data storage on the processor.

---

**Random Access Memory:**

- Memory is like a really big array
- Contains instructions for programs that are currently being executed.
- Stores any data a program may need.

**The two “sides” of memory:**

- Address side
- Data side (or Data @ Address)

NOTE: Everything here is technically in binary.

# Memory Layout Example


This example is used to show the type of data that can be found in memory.

<u>Addresses</u>	<u>Data @ Addresses</u>	
0x3000	ADD R1, R2, R0	LC-3 Instructions: Piece of some program in memory.
0x3001	HALT	
0x3002	0 <b>b</b> 0010000100010000	Random Data in Memory: Data used by a program currently being executed. <b>OR</b> Left over data from an old program previously executed.
0x3003	0x2110	
...	...	
0x300A	#8464	
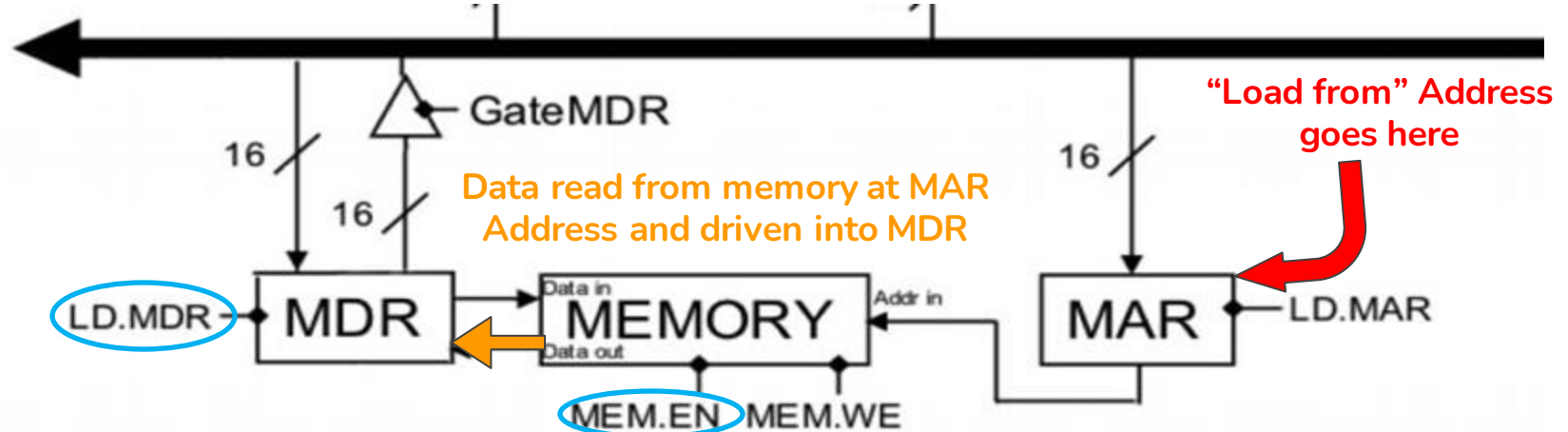
# Loading from Memory

Load data from memory:


- Place the **address** of where the data is located in MAR (Memory Address Register).
- Memory is **read** from that address and “driven” to the MDR (Memory Data Register). After that, the data moves to its destination register.


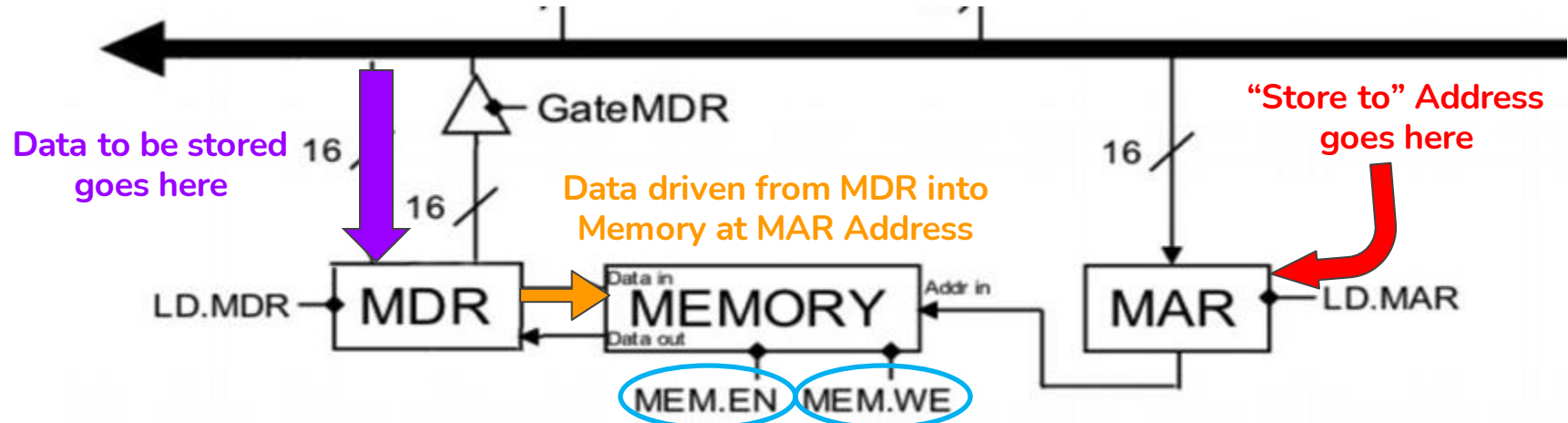
# Storing into Memory

Store data into memory:

- Data from a register is placed into the **MDR**.
- Address of where to store data is placed into the **MAR**.
- Data is stored in memory at the address specified by the **MAR**.







## Note

- Every piece of data in memory is just 16 bits of binary
- How does the LC-3 know...
  - Which addresses contain data that's an instruction?
  - Which addresses contain data that's an integer?
  - Which addresses contain data that's a character?
- Answer: it doesn't!

  
# ALU

- Two inputs:
  - SR1: Data from register
  - SR2: Data from register **OR** immediate value from the instruction
- Select bits come from Finite State Machine
  - 00  $\rightarrow A + B$
  - 01  $\rightarrow A \text{ AND } B$
  - 10  $\rightarrow \text{NOT } A$
  - 11  $\rightarrow \text{PASS } A \text{ (unchanged)}$
- Drives output onto bus
- Condition codes (CC)
  - Set when writing to general purpose registers, LD.CC flag
  - Only three possible states: 001, 010, 100
  - What do they each mean?


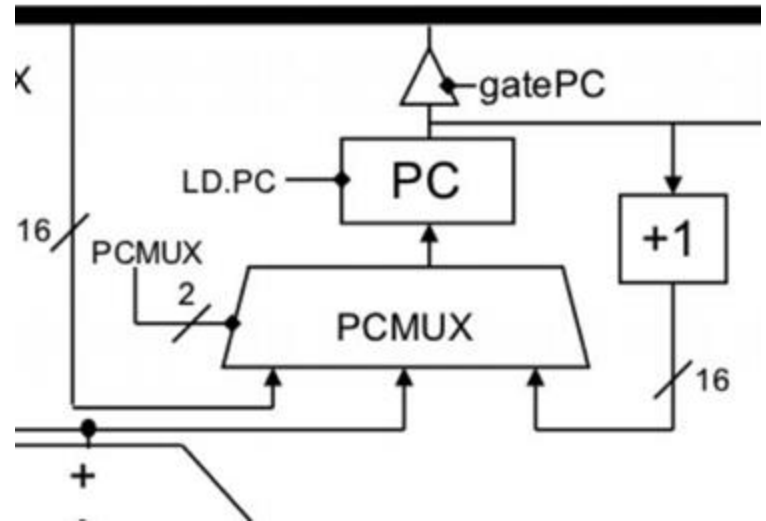
# PC

- Holds the current program counter – address of next instruction to execute
- Repeat that: "the address of the *next* instruction to execute"
- It does NOT hold:
  - The current instruction
  - The address of the current instruction
- Three ways to update PC
  - PC + offset
  - PC + 1
  - Given a value for the PC via the bus
- The "correct" way is selected through PCMux




# IR

- Instruction register – holds the **value** of the **current** instruction
- For example, the instruction ADD R3, R1, R2 may look like:

	0001	011	001	0	00	010
ADD	0001	DR	SR1	0	00	SR2

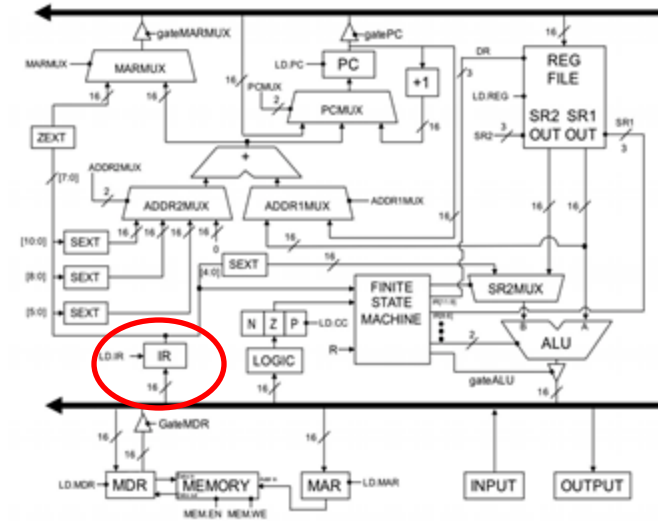- Having the correct value in the IR helps the FSM determine the current state and send the correct control signals
- A new value can be read from the bus (with signal LD.IR) and the current value is directly connected to relevant components






# LC3 Instruction Set

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
BR	0000	n	z	p	PCoffset9	

LD	0010	DR	PCoffset9			
LDI	1010	DR	PCoffset9			
LDR	0110	DR	BaseR	offset6		
LEA	1110	DR	PCoffset9			
NOT	1001	DR	SR	111111		
ST	0011	SR	PCoffset9			
STI	1011	SR	PCoffset9			
STR	0111	SR	BaseR	offset6		

# Executing Instructions

 

Instruction execution has three "stages", called *macrostates*


- Each macrostate is made of one or more *microstates* (1 per clock cycle)
- The microstates are the states in the microcontroller's state machine!

The macrostates are:


1. Fetch (3 clock cycles)
  - Load the next instruction from memory into the instruction register (IR)
  - Increment the PC
2. Decode (1 clock cycle)
  - The microcontroller looks at the instruction to figure out how to execute it
3. Execute (varies)
  - The microcontroller steps through several microstates and asserts the correct control signals to execute the instruction

**The book splits up executing instructions into seven phases. This is a more conceptual overview of how it works and is unrelated to the three macrostates.**


# Fetch: Part 1

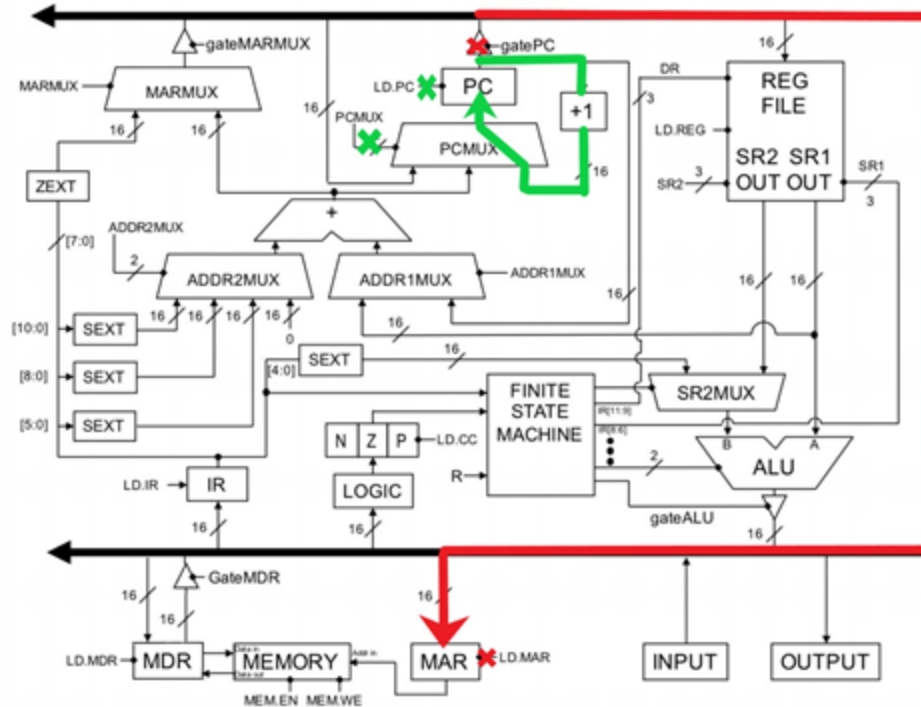

# Fetch: Part 2

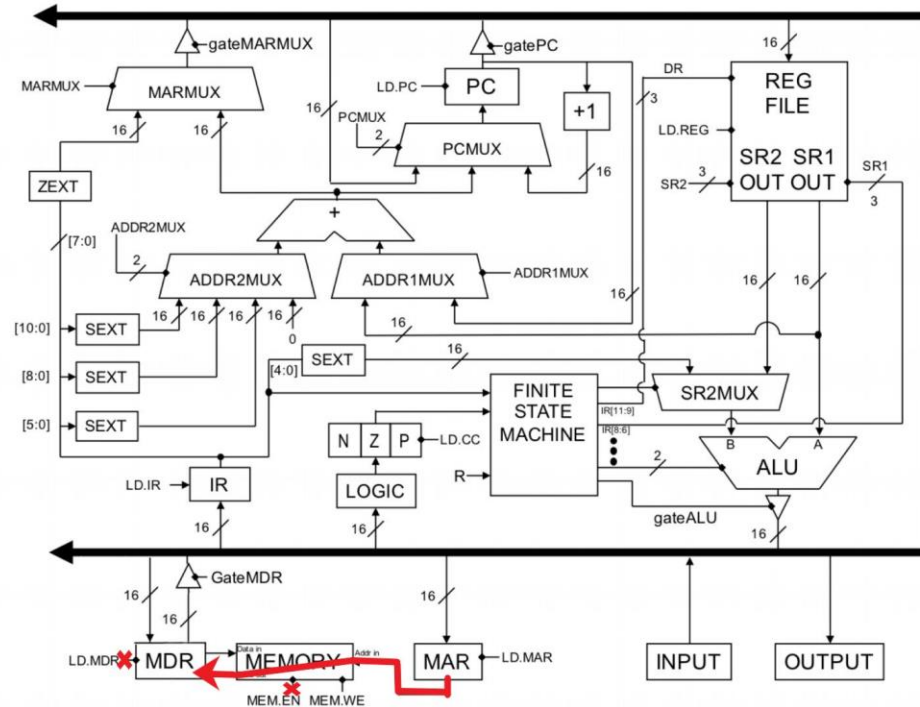


# Fetch: Part 3

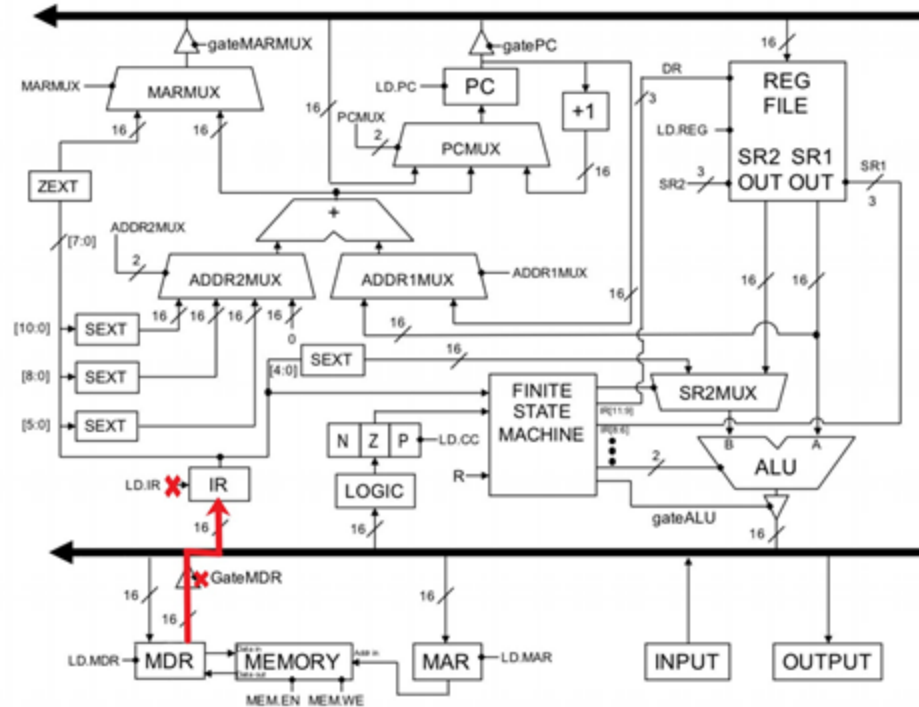




# What is MEM.EN used for?

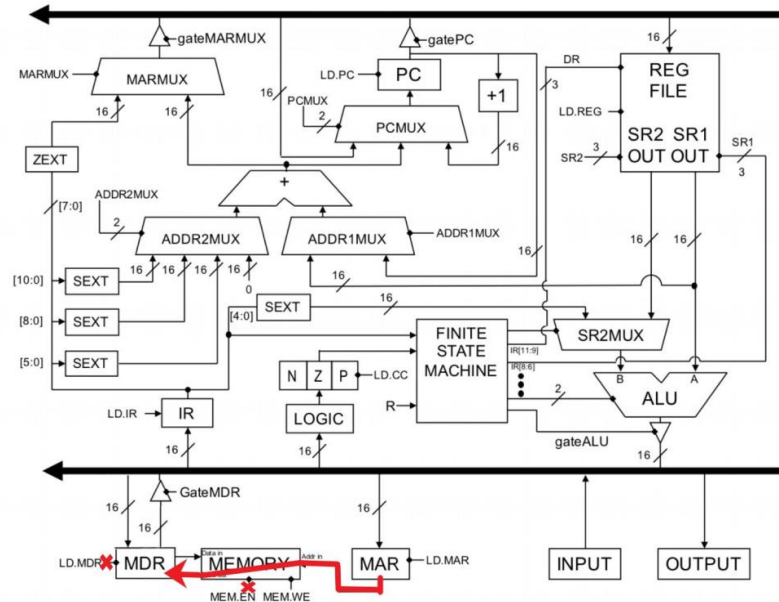


# Execute: immediate ADD

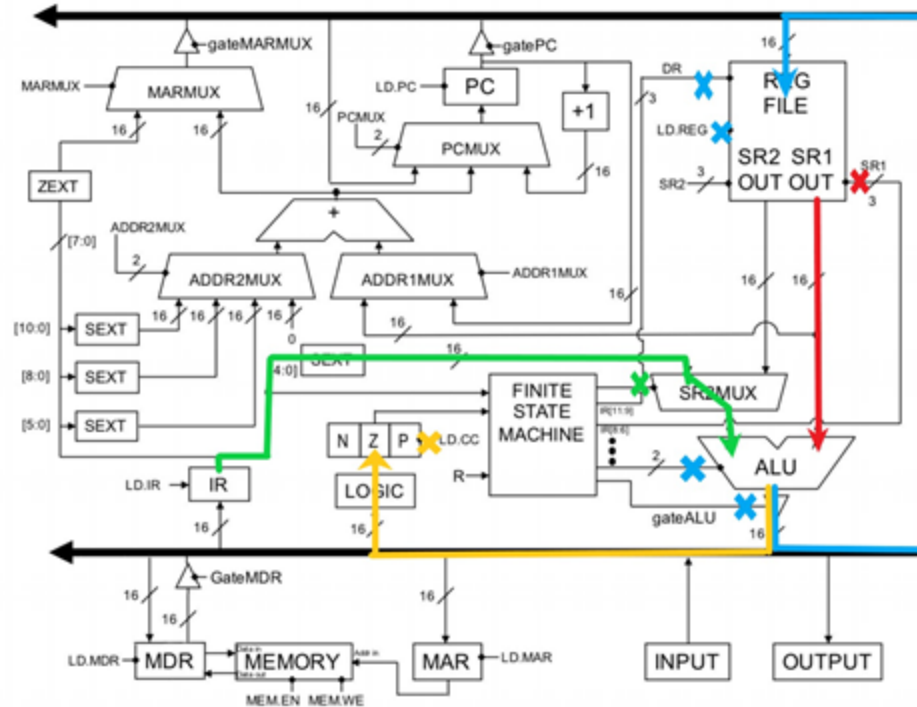





# Execute: STR (Part 1)

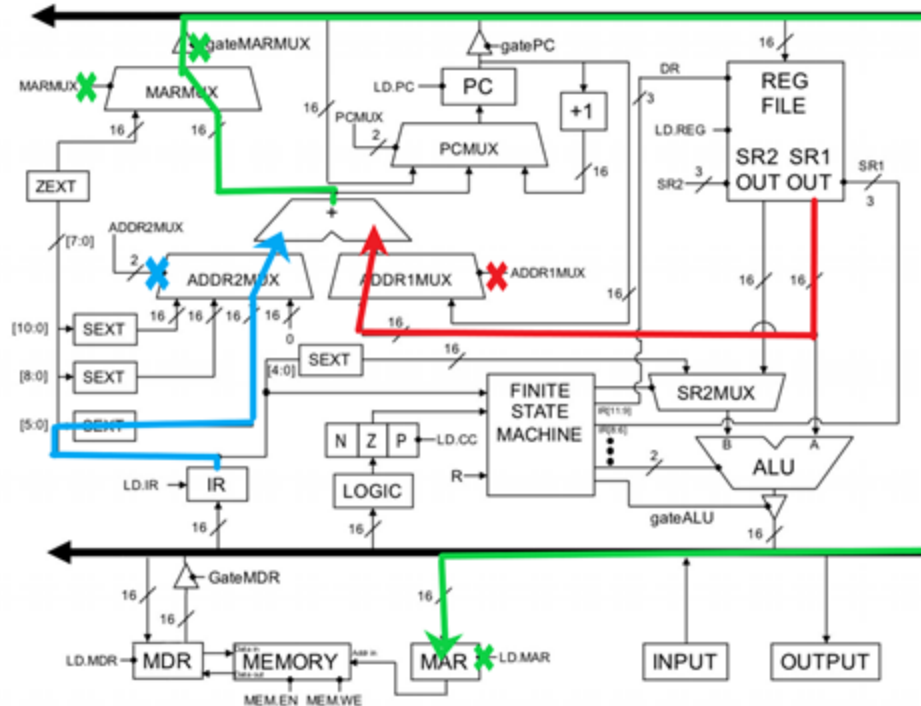



# Execute: STR (Part 3)

