

# Digital Logic I



- Transistors
- Logic Gates
  - NOT, OR, NOR, AND, NAND
  - DeMorgan's Law
  - Larger Gates
- Combinational Logic Circuits
  - Decoder, MUX, Full Adder, PLA,
  - Logical Completeness
- Simplification
  - Boolean
  - Karnaugh Maps
  - PLA/PGA



## Open Switch

No current can flow



## Closed Switch

Current can flow

# Our Story Begins



## George Boole



library.thinkquest.org

George Boole was an English mathematician, philosopher and logician. His work was in the fields of differential equations and algebraic logic, and he is now best known as the author of The Laws of Thought. Wikipedia

**Born:** November 2, 1815, [Lincoln](#)

**Died:** December 8, 1864, [Ballintemple, Cork](#)

**Spouse:** [Mary Everest Boole](#) (m. 1855)

**Children:** [Alicia Boole Stott](#), [Ethel Lilian Voynich](#), [Lucy Everest Boole](#), [Mary Ellen Boole Hinton](#), [Margaret Taylor](#)

**Awards:** Royal Medal

# Telegraph

## Samuel Morse



en.wikipedia.org

Samuel Finley Breese Morse was an American contributor to the invention of a single-wire telegraph system based on European telegraphs, co-inventor of the Morse code, and an accomplished painter. [Wikipedia](#)

**Born:** April 27, 1791, [Charlestown](#)

**Died:** April 2, 1872, [New York City](#)


**Education:** [Yale University](#), [Phillips Academy](#)

**Parents:** [Jedidiah Morse](#), [Elizabeth Ann Finley Breese](#)


**Siblings:** [Sidney Edwards Morse](#)



# Telegraph Schematic

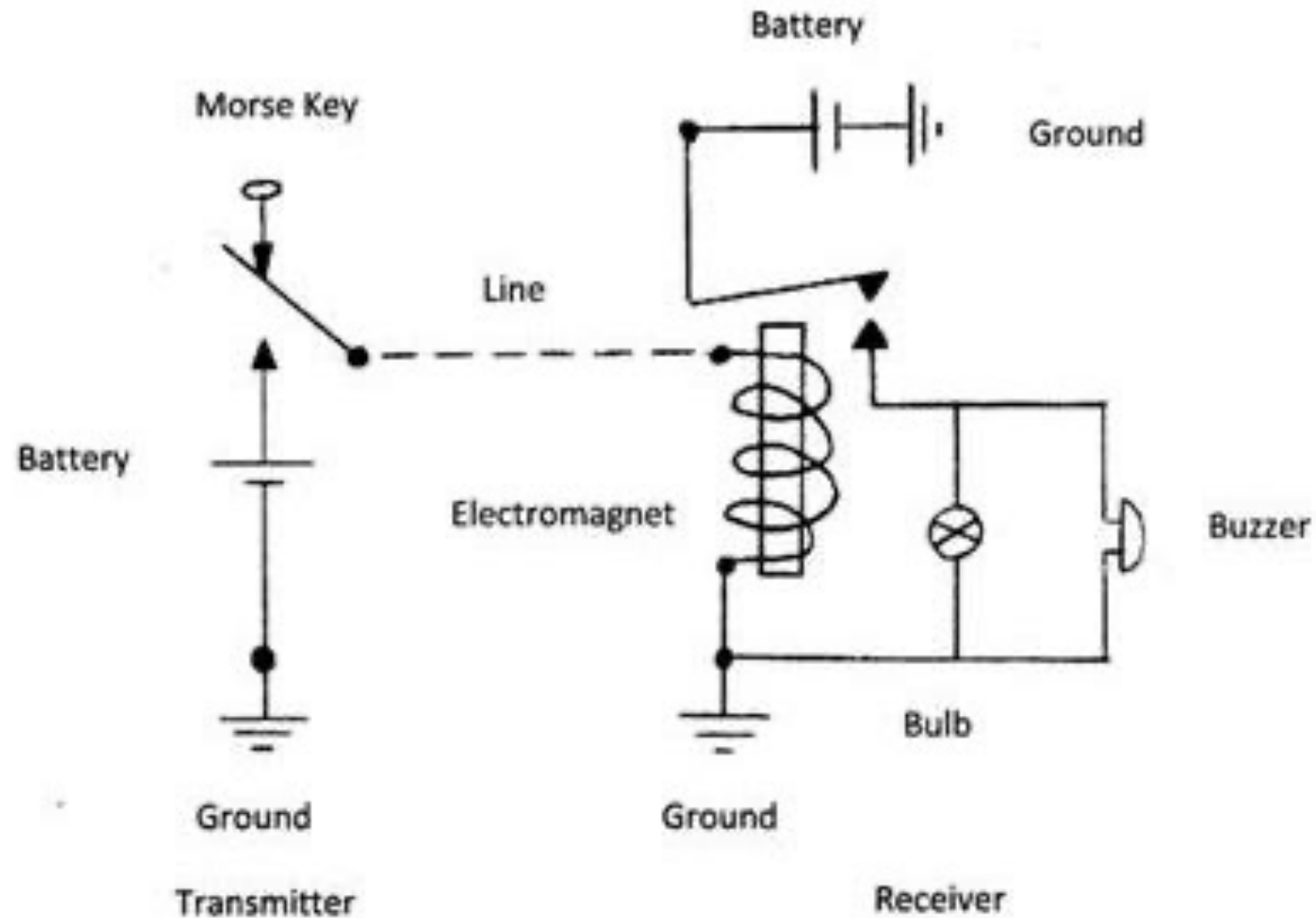


# Repeater

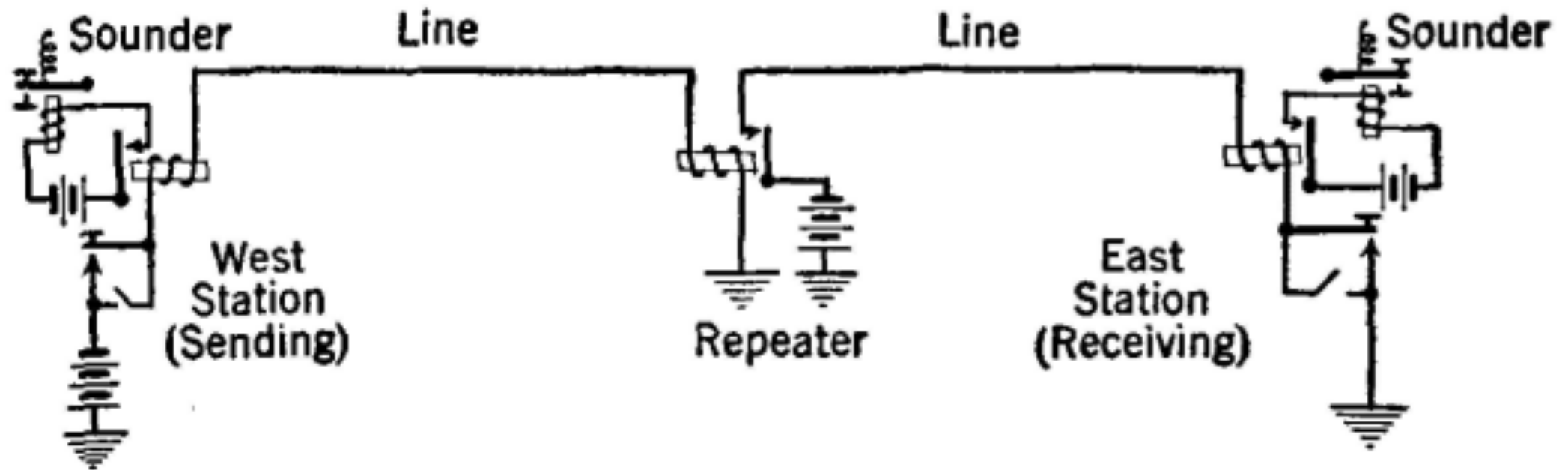




# Relay

 

# Relay

 

# Claude Shannon

## Claude Elwood Shannon



[en.wikipedia.org](https://en.wikipedia.org)

Claude Elwood Shannon was an American mathematician, electronic engineer, and cryptographer known as "the father of information theory". Shannon is famous for having founded information theory with one landmark paper published in 1948. [Wikipedia](#)

---

**Born:** April 30, 1916, [Petoskey](#)

---

**Died:** February 24, 2001, [Medford](#)

---


**Books:** [The mathematical theory of communication](#), Claude Elwood Shannon

---

**Education:** [Massachusetts Institute of Technology](#), [University of Michigan](#)

---

 **Awards:** IEEE Medal of Honor, National Medal of Science for Engineering, [More](#)



A SYMBOLIC ANALYSIS  
OF  
RELAY AND SWITCHING CIRCUITS

by

Claude Elwood Shannon  
B.S., University of Michigan  
1936


Submitted in Partial Fulfillment of the  
Requirements for the Degree of  
MASTER OF SCIENCE  
from the  
Massachusetts Institute of Technology  
1940

Signature of Author \_\_\_\_\_

Department of Electrical Engineering, August 10, 1937


Signature of Professor  
in Charge of Research \_\_\_\_\_

 Signature of Chairman of Department  
Committee on Graduate Students \_\_\_\_\_



But...

 
- Relays are
  - Slow
  - Good for hundreds of thousands of cycles
  - Wear out
  - Big
  - Noisy
- So...




# Diode
 
# Edison Effect (Thermionic Emission)

- Note that the electrons will only flow in one direction!
- If an AC power source replaces the anode battery, the current changes polarity twice each cycle
- Current will only flow during the parts of the sine wave where the charge is negative
- The resulting current is thus DC with current flowing every half-cycle
- We call this diode a **rectifier** when it's used to convert AC to DC power




**Electron flow**

 

**No current**




 

## Triode

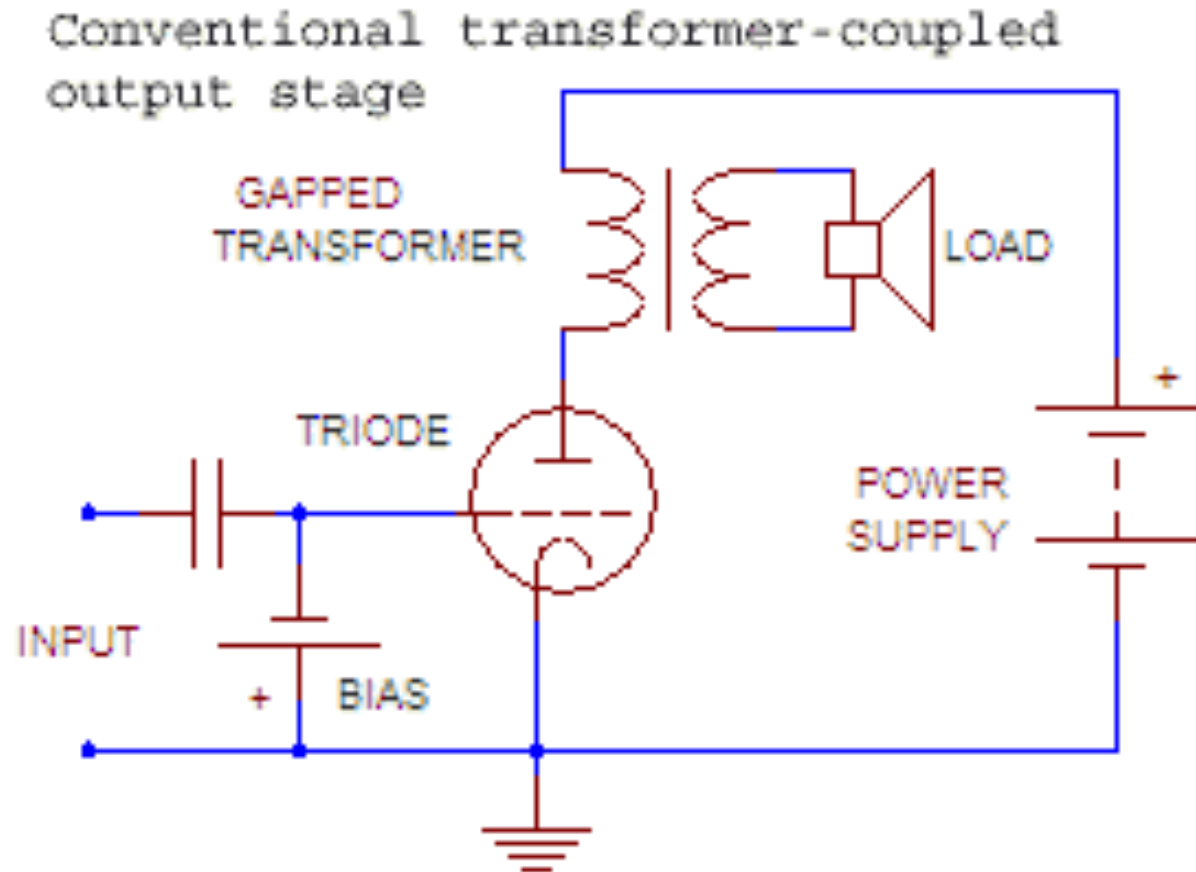
# Triode as Amplifier

- The input signal is a current from a microphone that represents the sound waves hitting the microphone
- The signal modulates the charge on the triode grid
- The charge applied to the grid permits or inhibits the flow of a larger current from the filament to the anode
- The output signal to the speaker is a higher current but proportional to the input signal



- Used as
  - Switches
  - Amplifiers
- In
  - Radio
  - Television
  - Stereo
  - Radar
  - Computers

## eniac vacuum tubes

 

Replacing a bad tube meant checking among ENIAC's 19,000 possibilities.


ENIAC

But...


- Tubes are
  - Hot
  - High power consumption
  - High voltages
  - Unreliable
  - Expensive
  - Consist of many individual components
- So...
 
# William Shockley


- Born February 13, 1910 Greater London, England, UK
- Died August 12, 1989 (aged 79) Stanford, California, US
- Nationality American
- Alma mater MIT, Caltech
- Known for
  - Point-contact transistor and BJT
  - Shockley diode equation
  - Read-Shockley equation
  - Shockley–Ramo theorem
  - Haynes-Shockley experiment
  - Shockley–Queisser limit
- Awards
  - Nobel Prize in Physics (1956)
  - Comstock Prize in Physics (1953)
  - Oliver E. Buckley Condensed Matter Prize (1953)
  - Wilhelm Exner Medal (1963)
  - IEEE Medal of Honor (1980)



So to save money...

 


# Transistors

 




# Different Switches

 

A physical switch

 


An electronic switch



Who made the connection that Boolean algebra expressions could be implemented by electric circuits?


- A. William Shockley
- B. Thomas Edison
- C. Claude Shannon
- D. John Ambrose Fleming



 


**Figure 3.2** The n-type MOS transistor
  
# Complementary Transistors



n-Type MOS



p-Type MOS

# Common Misconception: Digital Wires Have 3 (not 2) States!



- A wire with some designated voltage (e.g. +2.9 volts) can represent a logical 1.
- A wire with some designated voltage (e.g. 0 volts or ground) can represent a logical 0.
- A wire that is not connected to 2.9 volts or ground is said to be **floating** or in a **high impedance state** and its value can randomly vary from a logical 0 to 1.

# Transistor Comparison



## n-Type (normally open)

## p-Type (normally closed)


(normally)  
without power  
to the gate

  

with power  
to the gate

  


# N-type MOS FET\*

 


\*Metal Oxide Semiconductor Field Effect Transistor

# Gate Open

 




# Gate Closed

 
 
## n-Type (normally open)

You have an n-type transistor connected to 2.9v and 0v as shown. What voltage value will we measure at the drain?




- A. 0v
- B. 2.9v
- C. 1.45v
- D. Unknown




Because the gate is at 0v, the drain is disconnected from the source and is floating. We can't tell what value will be measured.


# N-Type FET

 

# CircuitSim N-Type MOS FET

 


# N-Type with Gate at +V

 


With the supply voltage applied to the device the transistor acts like a closed or connected switch

# N-Type with Gate at Ground

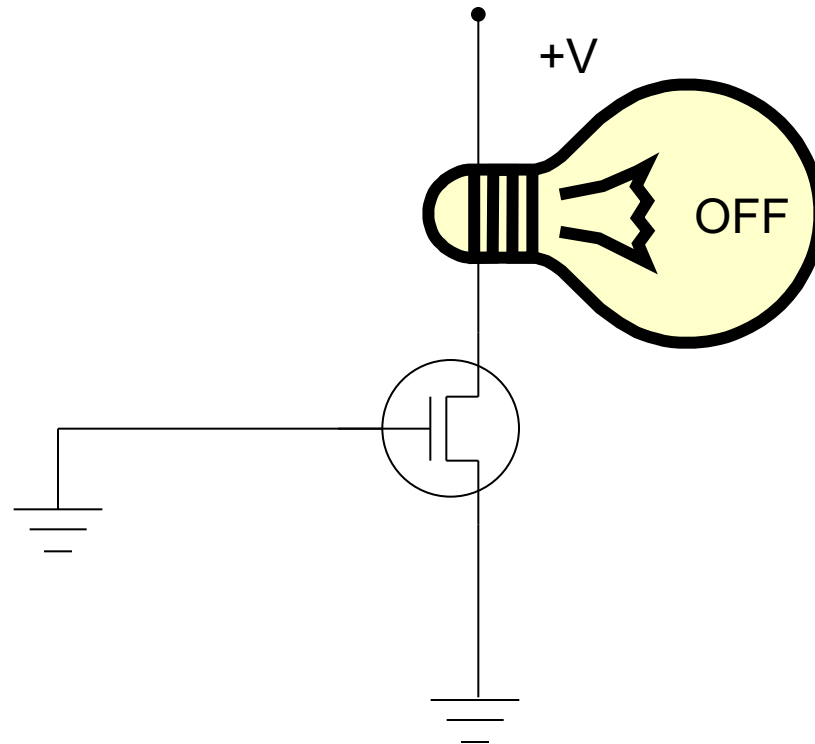


Open

# P-Type MOS FET

 


# CircuitSim P-Type MOS FET

 




## P-Type with Gate at +V

 

With the supply voltage applied to the device the transistor acts like a open or disconnected switch


# P-Type with Gate at Ground

 


Closed

# Logical Operations Revisited

A	NOT
0	1
1	0

 

A	B	AND
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	OR
0	0	0
0	1	1
1	0	1
1	1	1




A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0




A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0




A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


# Boolean Gate Representation

 


# NOT Gate (Inverter)

 


# NOR Gates...

 

## ...OR Gates

 

# NAND and AND Gates


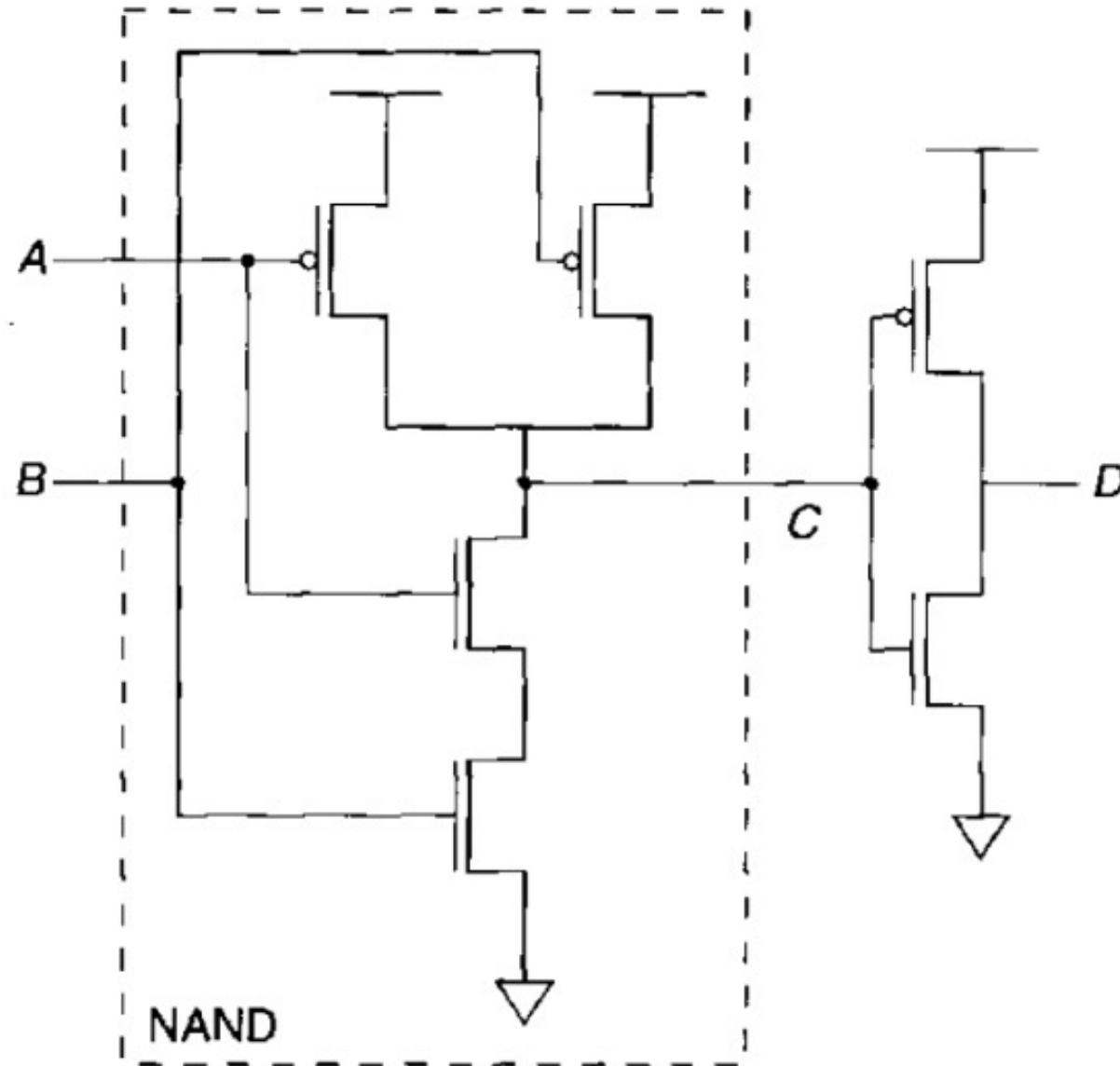





- Discrete transistors
  - Are still big
  - Use a lot of material to build
  - Use a lot of power (and hence generate a lot of heat); however smaller transistors need smaller amounts of power
  - Need a lot of individual connections, all of which are prone to failure
  - Are so useful that we need *lots* of them
- So...
  
# Digital Logic: Building Blocks


- The basic digital logic building blocks are available as pre-packaged self-contained integrated circuits.
- These chips are fast, inexpensive and easy to work with.
- Each chip contains 1-6 gates. Complicated designs can require thousands of gates and hundreds of chips.



6 NOT Gates  
74HC04

 

4 OR Gates  
74HC32

 


4 AND Gates  
74HC08

# DeMorgan's Law




➤  $(A'B')' = A+B$

➤  $(A'+B')' = AB$

 


A	B	A'	B'	A'B'	$(A'B')'$	A'+B'	$(A'+B')'$	A+B	AB
0	0	1	1	1	0	1	0	0	0
0	1	1	0	0	1	1	0	1	0
1	0	0	1	0	1	1	0	1	0
1	1	0	0	0	1	0	1	1	1



# Conte Bubble Theorem

   


# Larger Gates

 

ABCD

  

# Fan-In and Fan-Out

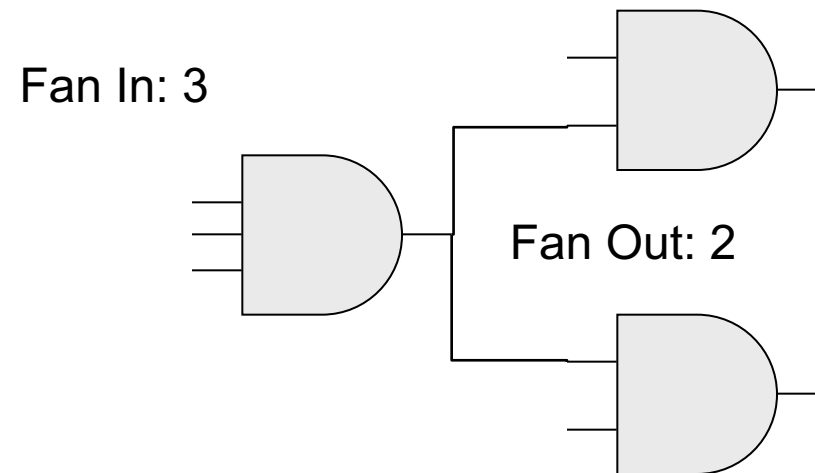

Warning

➤ Important concept approaching!

# Combinational Logic

- A combination of AND, OR, NOT (plus NAND & NOR)
- The same inputs always produce same output




# Whack-A-Mole!



Fun!



 

# Problem


- You have an  $n$  bit binary number which signifies which mole is selected. How do we electrically actuate the desired mole?



[Csim]



# Decoder

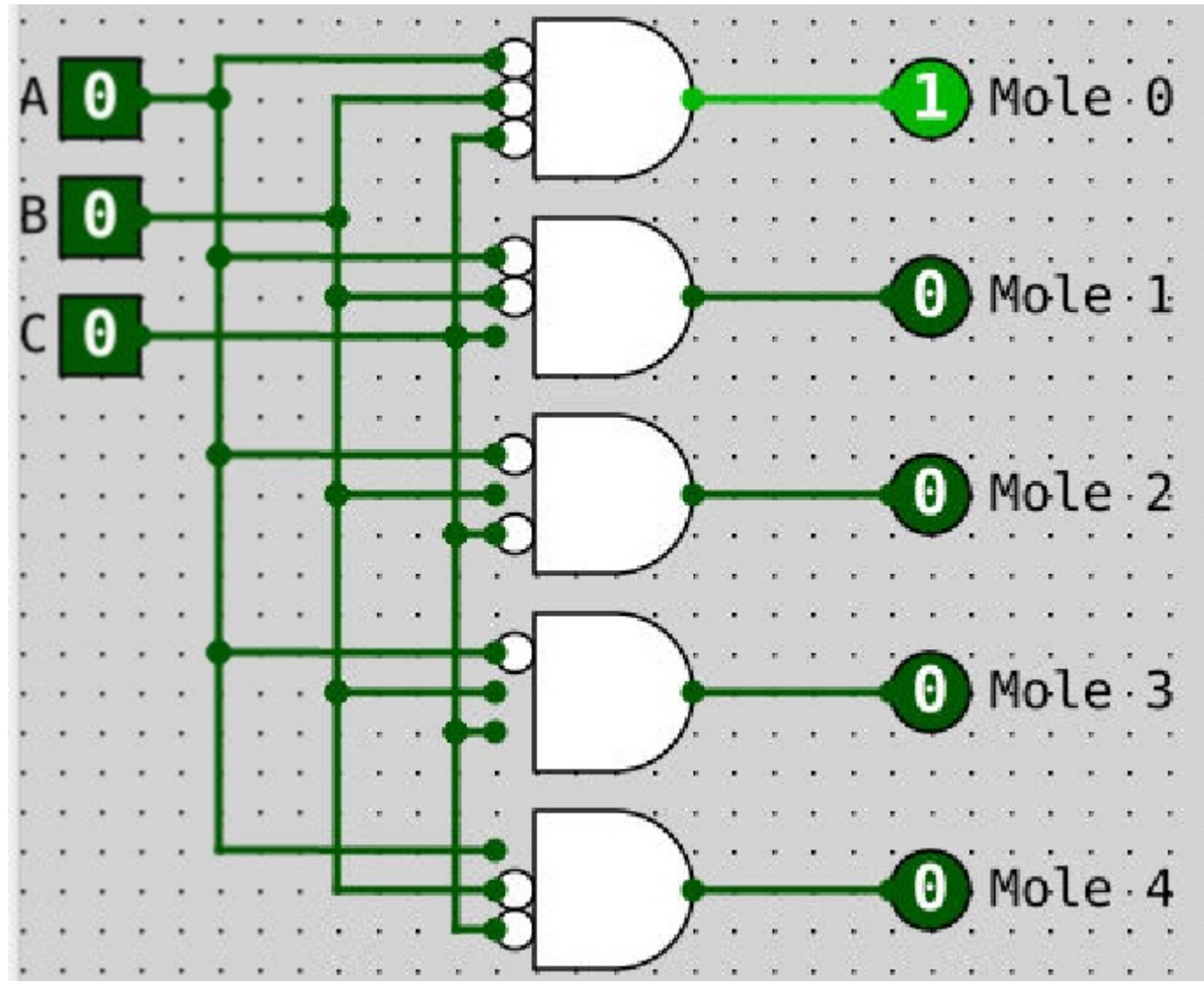

# Question

If you had a decoder with a 5 bit input (i.e. a 5 bit binary number) how many outputs at most could the decoder have?

$2^5$  possible  
input values

So a maximum  
of  $2^5 = 32$   
output values

A. 5

B. 10

C. 16

D. 32


E. 64



The winning number is  
53,122


# Question

If you have a decoder with  $n$  input bits (i.e. an  $n$  bit binary number) what is the most outputs the decoder could have?

- A.  $2n$
- B.  $n^2$
- C.  $2^n$  
- D. Cannot determine
- E. 4

 
# Problem

- You have  $m$  signals and you want to select the logical value on one of them, determined by a set of  $n$  control wires






# Multiplexor (MUX)

 


The basic multiplexor has


- A.  $n$  outputs,  $n$  control lines,  $2^n$  inputs
- B. 1 output,  $2n$  control lines,  $n$  inputs
- C. 1 output,  $n$  control lines,  $2^n$  inputs 
- D.  $2^n$  outputs, 2 control lines,  $n$  inputs
- E. 1 output, 4 control lines, 2 inputs

- No one will buy your new computer design unless it can do at least some math, say, like adding!


# Simple Adder

 

# Half Adder

 

# Full Adder

 

# Truth in Adding


A	B	Carry In	Out	Carry Out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

# Truth in Adding

A	B	Carry In	Out	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Full Adder

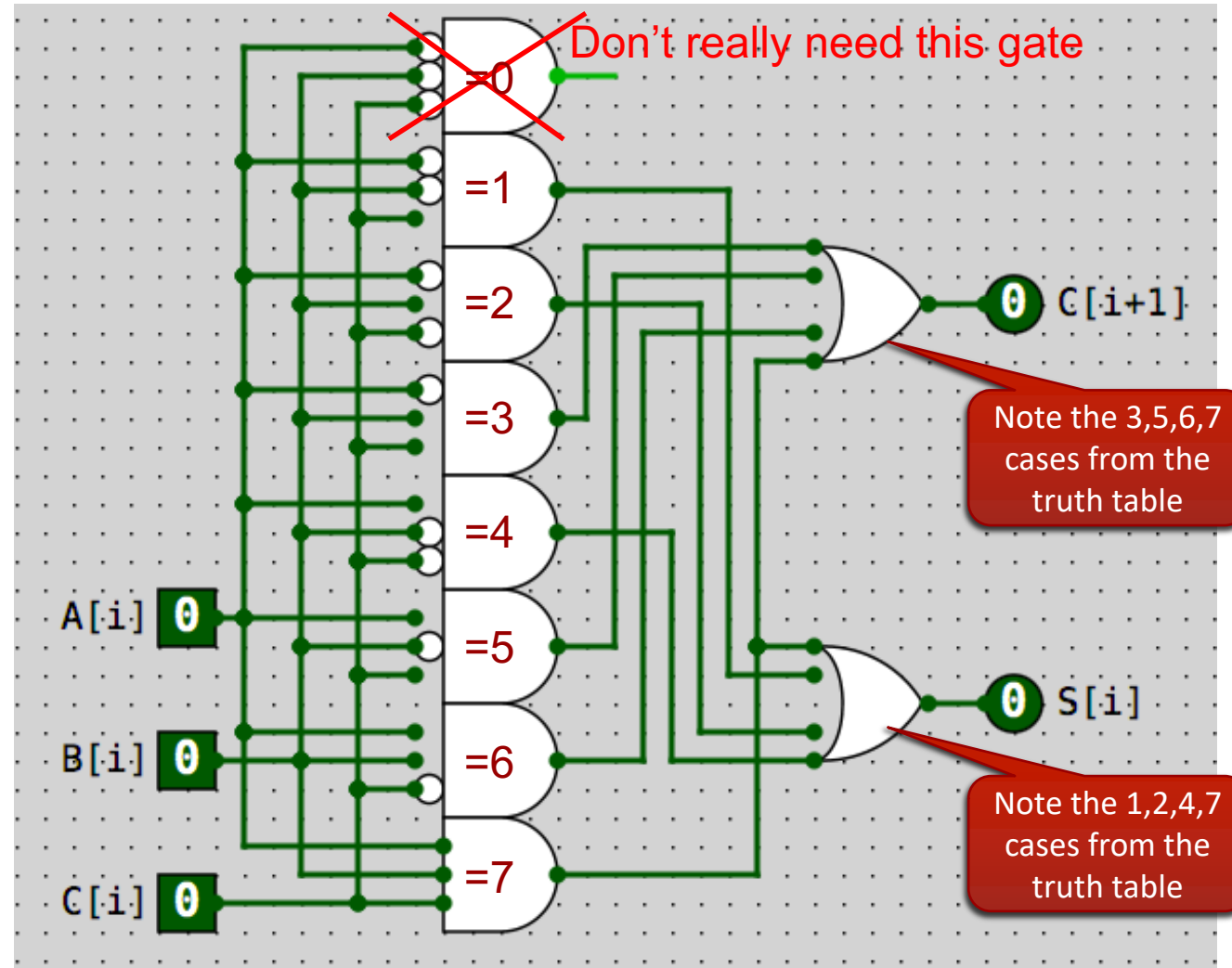

# The No Thinking Method!

Go buy a full-adder IC chip from Digi-Key.

# Boolean Simplification



# Boolean Simplification

## *Basic Boolean algebraic properties*

### Additive

$$A + B = B + A$$

$$A + (B + C) = (A + B) + C$$

$$A(B + C) = AB + AC$$

### Multiplicative

$$AB = BA$$

$$A(BC) = (AB)C$$

$$\overline{\overline{A}} = A$$

## *Basic Boolean algebraic identities*

### Additive

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \overline{A} = 1$$

### Multiplicative

$$0A = 0$$

$$1A = A$$

$$AA = A$$

$$A\overline{A} = 0$$



## *Useful Boolean rules for simplification*

$$A + AB = A$$

$$A + \overline{A}B = A + B$$

$$(A + B)(A + C) = A + BC$$

## *DeMorgan's Laws*

  

Simplify the following Boolean expression:

$$E = ABCD + BC + A'BC$$

$$(E = A \& B \& C \& D \mid B \& C \mid \sim A \& B \& C)$$



A. BC

B. A

C. A'C

D. AD

E. D

$$E = ABCD + BC + A'BC$$

[use identity:  $a + ab = a$ ]

$$ABCD + BC \rightarrow BC$$

$$BC + A'BC \rightarrow BC$$

$$E = BC$$

$$AB + A' \rightarrow B + A'$$

A	B	AB	A'	AB+A'	B+A'
0	0	0	1	1	1
0	1	0	1	1	1
1	0	0	0	0	0
1	1	1	0	1	1

# Consider This Circuit


A	B	C	OUT
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

# Truth Table to Circuit

- An AND gate for every line in the truth table (i.e. build a decoder) connected to the inputs
- An OR gate connecting the AND gates for the lines that have 1 in their output column



# Implement the Truth Table

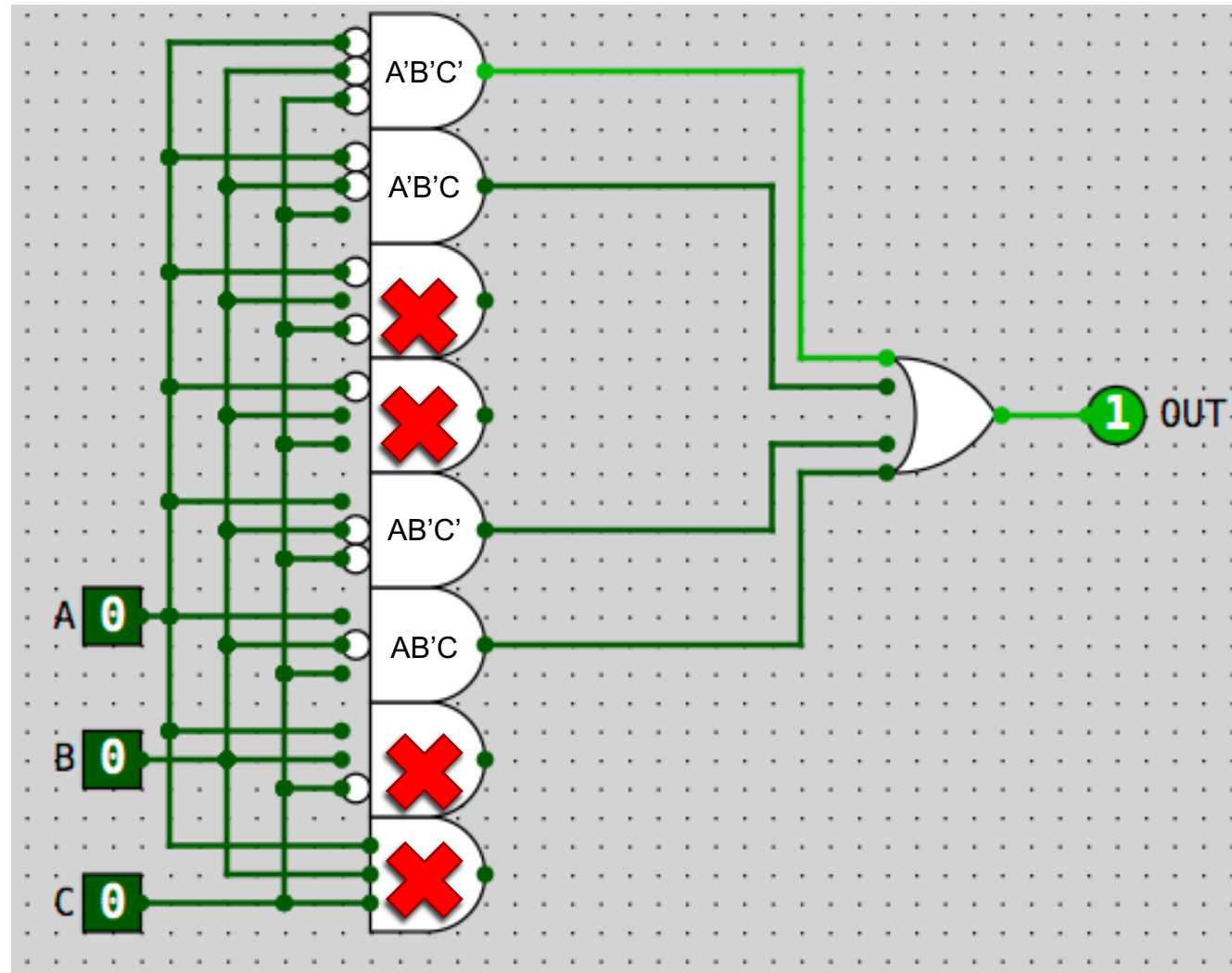

$$F = A'B'C' + A'B'C + AB'C' + AB'C$$

# Circuit to Boolean Expression / Truth Table

- Circuit to Boolean Expression
- If it's a sum-of-products circuit then
  - Each AND gate generates a term with the input conditions that yield a 1 from the AND gate (times)
  - All of the terms are ORed together (plus)
- Circuit to Truth Table
  - Each AND gate represents one row of your truth table (inputs)
  - Each OR gate represents one output column of your truth table
    - All of the inputs that produce a 1 output are tied to that OR gate

# Classic Simplification

$$\Rightarrow F = A'B'C' + A'B'C + AB'C' + AB'C$$


$$\Rightarrow F = A'B'(C'+C) + AB'(C'+C)$$

$$\Rightarrow F = A'B' + AB'$$

$$\Rightarrow F = B'(A'+A)$$

$$\Rightarrow F = B'$$

# Quite a Simplification, No?

 

- We are used to writing sum-of-products with algebraic polynomials, e.g.

$$X^3 + 4X^2 + 2X + 12$$

- Turns out that truth tables (and other forms) naturally yield boolean expressions in sum-of-products form, e.g.

$$ABC + ABC' + A'BC + A'B'C'$$

- This turns out to be very convenient for implementing circuits

# Equivalence!

- Boolean Expression
  - Truth Table
  - Combinational Circuit
  - Karnaugh Map
- 
- You can change between ANY of these forms without losing information!

# Karnaugh Maps

➤ Resources:

➤ <http://electronics-course.com/karnaugh-map>

➤ <http://www.32x8.com/circuits7>

- Can you convert
  - A Karnaugh map to a combinational circuit?
  - A truth table to a Karnaugh map
  - A truth table to a combinational circuit?
  - A Boolean expression into a Karnaugh map?
  - A Boolean expression into a truth table?
  - A truth table into a Boolean expression?



# Truth Table

A	OUT
0	x
1	y

# 1 Variable Karnaugh Map

$A'$	$A$
What is the output if $A$ is false?	What is the output if $A$ is true?

What does it mean if both boxes contain 1?

# 1 Variable Karnaugh Map

$A'$	$A$
$x$	$y$

What does it mean if both boxes contain 1?

Map:  $OUT = A'$

$A'$	$A$

Truth Table:  $OUT = A'$

A	OUT
0	1
1	0

Map:  $OUT = A'$

$A'$	$A$
1	0

## 2-Variable Truth Table

A	B	OUT
0	0	$X_0$
0	1	$X_1$
1	0	$X_2$
1	1	$X_3$

## 2-Variable K-Map

	$B'$	$B$
$A'$	What is the output if both A and B are false?	What is the output if A is false and B is true?
$A$	What is the output if A is true and B is false?	What is the output if both A and B are true?



## 2-Variable K-Map

	$B'$	$B$
$A'$	$X_0$	$X_1$
$A$	$X_2$	$X_3$

Map:  $OUT = A'B' + AB$

	$B'$	$B$
$A'$		
$A$		

$$\text{Map: } \text{OUT} = A'B' + AB$$

	$B'$	$B$
$A'$	1	0
$A$	0	1

Can this expression be simplified?

$$\text{Map: } \text{OUT} = A'B' + AB'$$

	$B'$	$B$
$A'$		
$A$		

$$\text{Map: } \text{OUT} = A'B' + AB'$$

	$B'$	$B$
$A'$	1	0
$A$	1	0

Can this expression be simplified?

Which of these conversions between forms of a circuit are allowed because the forms are equivalent?

- A. A Karnaugh map to a combinational circuit
- B. A truth table to a Karnaugh map
- C. A truth table to a combinational circuit
- D. A Boolean expression into a Karnaugh map
- E. A Boolean expression into a truth table
- F. All of the above

- Suppose you had to give a series of 3 bit codes to disarm the detonation sequence of a nuclear device you were sitting on.
- There would be 8 codes and they had to go in a certain sequence picked by you.
- Any deviation would result in an immediate detonation of the nuclear device
- What codes in what order do you use?

# Classic Sequence

000

001

010

011

100

101

110

111



Two switches change at once!  
Can you get the timing perfect?  
Boom!



# Gray Code Sequence

000

001

011

010

110


111

101


100

} Only one switch per transition!  
All the way to the end!  
No boom!

# Optical Encoder

 


# Gray Code Optical Encoder

 
 
# 3-bit Gray Code

000  
001  
011  
010  
110  
111  
101  
100



## 2-bit Gray Code

00

01

11

10

This is the one you need to remember.

# 4-bit Gray Code

0000  
0001  
0011  
0010  
0110  
0111  
0101  
0100  
1100  
1101  
1111  
1110  
1010  
1011  
1001  
1000

Let's Revisit:  $OUT = A'B' + AB'$

	$B'$	$B$
$A'$	1	0
$A$	1	0

Each box differs from the adjacent boxes by exactly one bit!

## Let's Revisit: $OUT = A'B' + AB'$

	$B'$	$B$
$A'$	1	0
$A$	1	0

- $A'B'$  to  $A'B$  differs by 1 bit
- $A'B$  to  $AB$  differs by 1 bit
- $AB$  to  $AB'$  differs by 1 bit
- $AB'$  to  $A'B'$  differs by 1 bit
- This means that two adjacent 1 bits tell us that a variable can be removed from two terms
- Since there are one bits in the  $B'$  column, that tells us that both  $A$  and  $A'$  are present and the two terms can be consolidated to just the  $B'$  value:

$$OUT = B'$$



# 3-Variable Truth Table

A	B	C	OUT
0	0	0	$X_0$
0	0	1	$X_1$
0	1	0	$X_2$
0	1	1	$X_3$
1	0	0	$X_4$
1	0	1	$X_5$
1	1	0	$X_6$
1	1	1	$X_7$

Map:  $A'B'C + A'BC + ABC$

	<b>B' C'</b> (00)	<b>B' C</b> (01)	<b>BC</b> (11)	<b>BC'</b> (10)
<b>A'</b> (0)	$X_0$	$X_1$	$X_3$	$X_2$
<b>A</b> (1)	$X_4$	$X_5$	$X_7$	$X_6$

$$\text{Map: } A'B'C + A'BC + ABC$$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	0	1	1	0
$A$	0	0	1	0

Can this expression be simplified?

$$\text{Map: } A'B'C + A'BC + ABC$$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	0	1	1	0
$A$	0	0	1	0

Can this expression be simplified?

# How Does the Map Remove Variables?

- $A'B'C + A'BC + ABC$
- Two adjacent 1s in the map means there is an  $x + x'$  in the formula; the map tells us where
- $A'C(B' + B) + ABC$
- $A'C + ABC$

Map:  $A'C + ABC$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	0	1	1	0
$A$	0	0	1	0

Can this expression be simplified:  $A'C + BC$

# How Does the Map Remove Variables?

➤  $A'B'C + A'BC + ABC$

➤ Two adjacent 1s in the map means there is an  $x + x'$  in the formula; the map tells us where

➤  $A'C(B' + B) + ABC$

➤  $A'C + ABC$

➤  $C(A' + AB)$

➤  $C(A' + B)$

➤  $A'C + BC$

$$\text{Map: } A'B'C' + ABC' + AB'C' + A'BC'$$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	$X_0$	$X_1$	$X_3$	$X_2$
$A$	$X_4$	$X_5$	$X_7$	$X_6$




$$\text{Map: } A'B'C' + ABC' + AB'C' + A'BC'$$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	1	0	0	1
$A$	1	0	0	1

Can this expression be simplified?

Wrap!

 

$$\text{Map: } A'B'C' + ABC' + AB'C' + A'BC'$$

	$B' C'$	$B' C$	$BC$	$BC'$
$A'$	1	0	0	1
$A$	1	0	0	1

Expression simplifies to  $C'$

# 4-Variable Truth Table

A	B	C	D	OUT
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	



A \ B \ CD				
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10



# 4-Variable K-Map

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$				
$AB$				
$AB'$				

# 4-Variable Truth Table

A	B	C	D	OUT
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		CD			
		00	01	11	10
AB	00	0	1	3	2
	01	4	5	7	6
	11	12	13	15	14
	10	8	9	11	10

Map:  $A'B'C'D' + AB'CD' + AB'C'D' + A'B'CD'$

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$				
$AB$				
$AB'$				

A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Map:  $A'B'C'D' + AB'CD' + AB'C'D' + A'B'CD'$

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$	1			1
$A'B$				
$AB$				
$AB'$	1			1

Can this expression be simplified?



A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Map:  $A'B'C'D' + AB'CD' + AB'C'D' + A'B'CD'$

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$	1			1
$A'B$				
$AB$				
$AB'$	1			1

Simplifies to  $B'D'$

A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Each Pair Eliminates 1 Variable

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$	1			1
$AB$		1		
$AB'$		1		

Simplifies to  $A'BD' + AC'D$

A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Eliminates 2 Variables

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$				
$AB$		1	1	
$AB'$		1	1	

Simplifies to  $AD$

A \ B \ CD				
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Eliminates 3 Variables

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$	1			1
$A'B$	1			1
$AB$	1			1
$AB'$	1			1

Simplifies to  $D'$

A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Eliminates 3 Variables

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$	1	1	1	1
$AB$	1	1	1	1
$AB'$				

Simplifies to B

A \ B	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Don't care: Eliminates 3 Variables

	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$				
$A'B$	1	1	1	1
$AB$	X	1	1	1
$AB'$	X			

# Five Variable

E'	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

E	C'D'	C'D	CD	CD'
A'B'				
A'B				
AB				
AB'				

# 6 Variable

	$F'$	$F$																																																		
$E'$	<table><tr><td></td><td><math>C'D'</math></td><td><math>C'D</math></td><td><math>CD</math></td><td><math>CD'</math></td></tr><tr><td><math>A'B'</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>A'B</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB'</math></td><td></td><td></td><td></td><td></td></tr></table>		$C'D'$	$C'D$	$CD$	$CD'$	$A'B'$					$A'B$					$AB$					$AB'$					<table><tr><td></td><td><math>C'D'</math></td><td><math>C'D</math></td><td><math>CD</math></td><td><math>CD'</math></td></tr><tr><td><math>A'B'</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>A'B</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB'</math></td><td></td><td></td><td></td><td></td></tr></table>		$C'D'$	$C'D$	$CD$	$CD'$	$A'B'$					$A'B$					$AB$					$AB'$				
	$C'D'$	$C'D$	$CD$	$CD'$																																																
$A'B'$																																																				
$A'B$																																																				
$AB$																																																				
$AB'$																																																				
	$C'D'$	$C'D$	$CD$	$CD'$																																																
$A'B'$																																																				
$A'B$																																																				
$AB$																																																				
$AB'$																																																				
$E$	<table><tr><td></td><td><math>C'D'</math></td><td><math>C'D</math></td><td><math>CD</math></td><td><math>CD'</math></td></tr><tr><td><math>A'B'</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>A'B</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB'</math></td><td></td><td></td><td></td><td></td></tr></table>		$C'D'$	$C'D$	$CD$	$CD'$	$A'B'$					$A'B$					$AB$					$AB'$					<table><tr><td></td><td><math>C'D'</math></td><td><math>C'D</math></td><td><math>CD</math></td><td><math>CD'</math></td></tr><tr><td><math>A'B'</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>A'B</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB</math></td><td></td><td></td><td></td><td></td></tr><tr><td><math>AB'</math></td><td></td><td></td><td></td><td></td></tr></table>		$C'D'$	$C'D$	$CD$	$CD'$	$A'B'$					$A'B$					$AB$					$AB'$				
	$C'D'$	$C'D$	$CD$	$CD'$																																																
$A'B'$																																																				
$A'B$																																																				
$AB$																																																				
$AB'$																																																				
	$C'D'$	$C'D$	$CD$	$CD'$																																																
$A'B'$																																																				
$A'B$																																																				
$AB$																																																				
$AB'$																																																				



Given the following K-map, what is the simplified expression it represents?


	$C'D'$	$C'D$	$CD$	$CD'$
$A'B'$	1	1		
$A'B$	1	1	1	1
$AB$			1	1
$AB'$	X	1		

- A.  $AD+BC+CD'$
- B.  $A'C'+CB+C'B'$  ←
- C.  $A'C'+CB+AB'C'$
- D.  $A'C'+CB+AB'C'D$
- E.  $ABC'+B'C$

# Remember: Same Data, Different Form

- Combinational Logic Circuit
- Boolean Expression
- Truth Table
- Karnaugh Map
 
# Can You Convert Any of These to Any Other?




# Strategy for 4-variable K-Maps

- Find a box around 16 1s.
  - If so, you are done.
- Find boxes around groups of 8 1s.
  - If no 1s are left, you are done.
- Find boxes around groups of 4 1s.
  - If no 1s are left, you are done.
- Find boxes around groups of 2 1s.
  - If no 1s are left, you are done.
- Find boxes around groups of single 1s.
- Done: Now write a term for every box you drew.
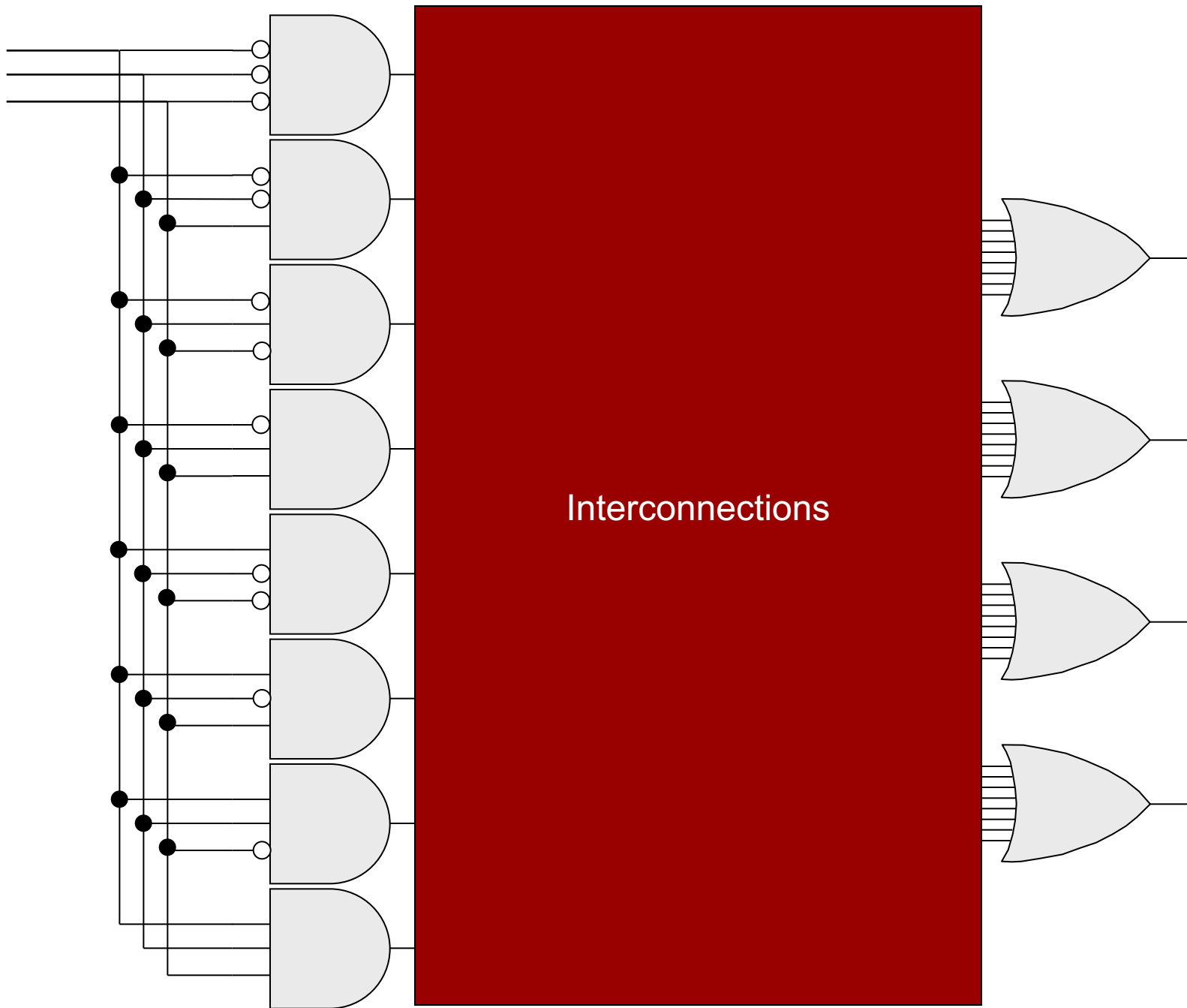
# Some Automation

- Try <http://32x8.com>
- Choose “4 variables” and “Kmap with Don’t cares” input option
- Watch it draw the circuits directly from the Kmaps

- Given a truth table we can implement it using output using a series of NOT gates, AND gates and then OR gates (remember sum-of-products?)
- We need  $2^n$  AND gates where  $n$  is the number of inputs
  - How many rows does the truth table have?
- We need one OR gate for each output
- General purpose ***Programmable Logic Array or (Field) Programmable Gate Array*** devices exist for this purpose



Decoder

AND gates

OR gates



- Transistors
- Logic Gates
  - NOT, OR, NOR, AND, NAND
  - DeMorgan's Law
  - Larger Gates
- Combinational Logic Circuits
  - Decoder, MUX, Full Adder, PLA,
  - Logical Completeness
- Simplification
  - Boolean
  - Karnaugh Maps
  - PLA/PGA