
CS 2110 - Lab 6

LC-3 Datapath & Tracing

Wednesday, June 8, 2022





Lab Assignment: LC3 Quiz!

- 1) Go to Quizzes on Canvas
- 2) Select Lab 06, password: **Fetch**
- 3) Get a 100% to get attendance!
 - a) Unlimited attempts
 - b) Collaboration is **allowed**!
 - c) Ask your TAs for help :)



Homework 3

- Released!
- **Due Monday, June 13th at 11:59 PM**
- Files available on Canvas
- Submit on Gradescope (unlimited submissions)



Homework 4

- Released on Friday, June 10th
- **Due Monday, June 20th at 11:59 PM**
- Files available on Canvas
- Submit on Gradescope (unlimited submissions)
- Will be demoed (logistics announced soon)




Quiz 2

- **Next Wednesday, June 15th**
- Quiz opens at your assigned lab time (unless you have already established a different time with your professor)
- Full 75 minutes to take the quiz!
- After the quiz, you will join lab for the remaining period.
- A topic list will be posted on Canvas




Timed Lab 2

- Scheduled on Wednesday June 22nd
- 75 minutes to complete at the beginning of lab, then lab will be resumed.
- Will cover HW4 Material primarily
 - Please have Docker working on the device you bring to Lab! If you have any trouble, please see a TA ASAP
 - If you need outlet priority, please let a TA know ASAP
 - You may use any submitted homework files during the timed lab
 - Unlimited submissions throughout the TL period.

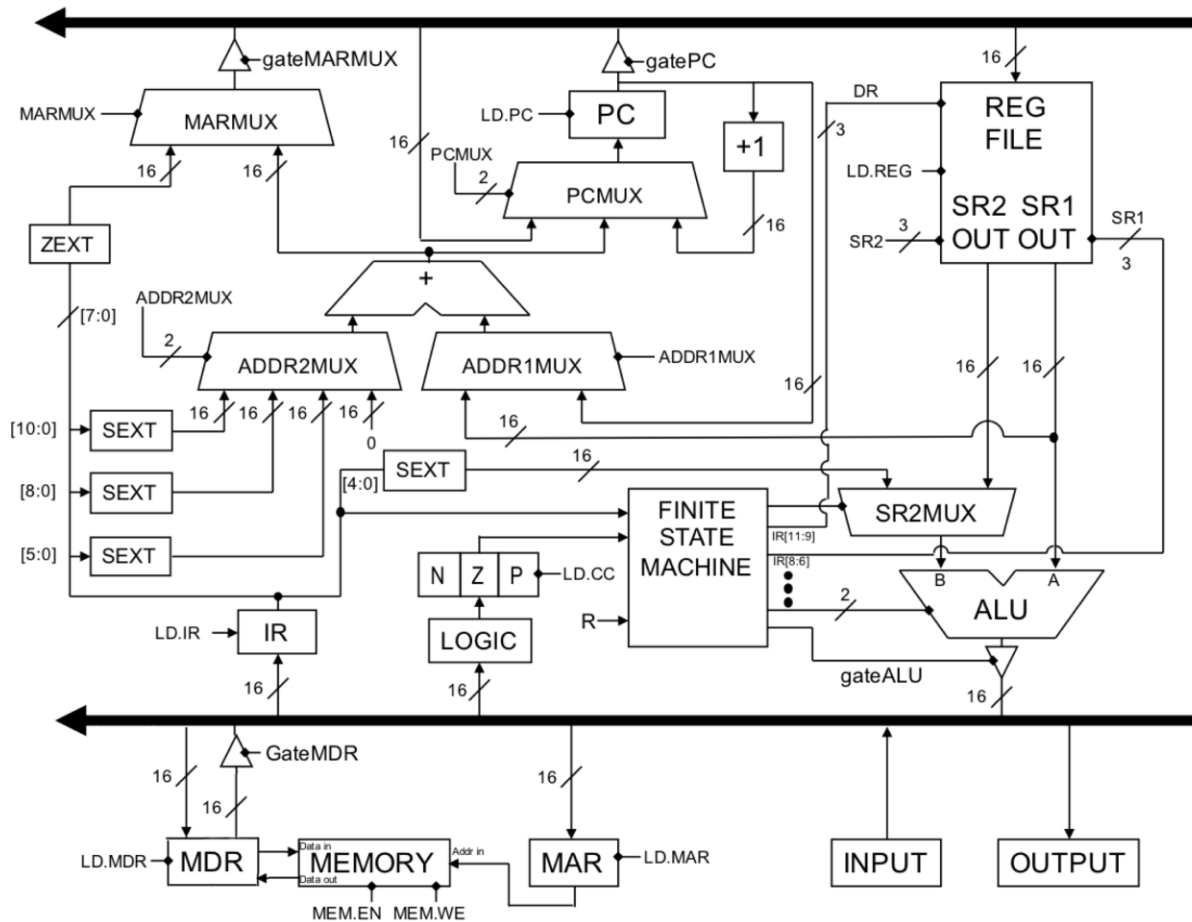


LC-3 Components

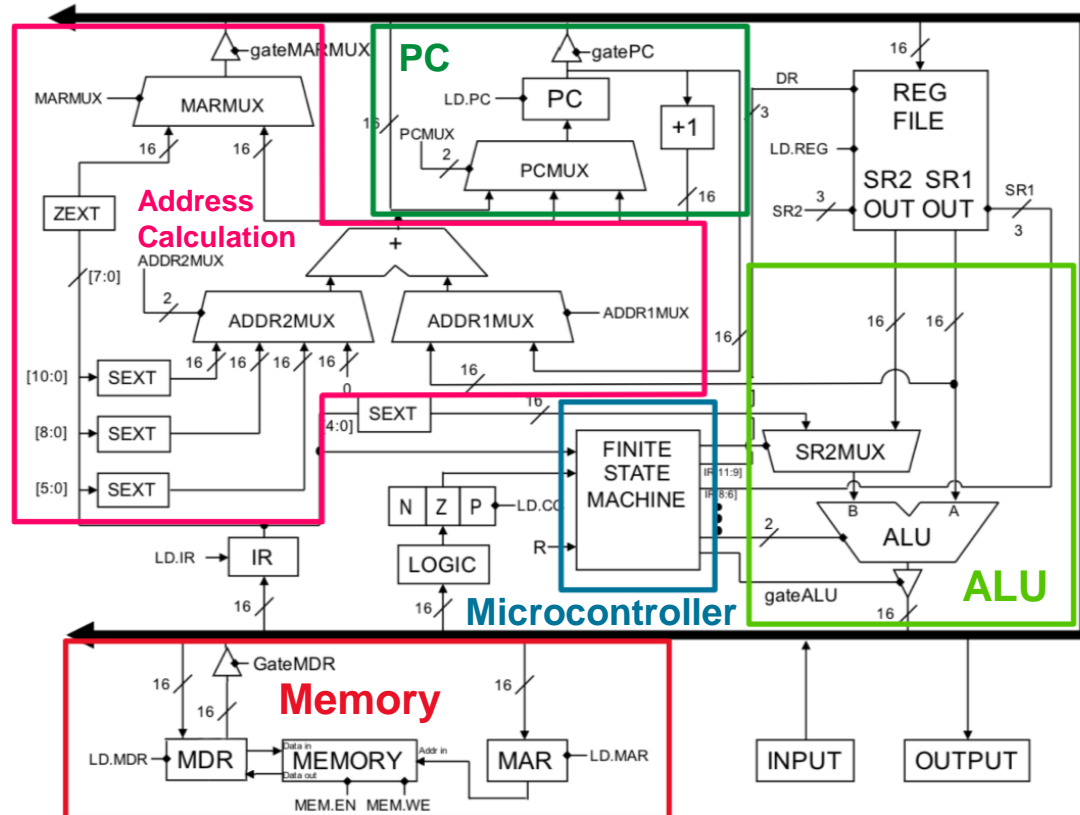


Control Signals

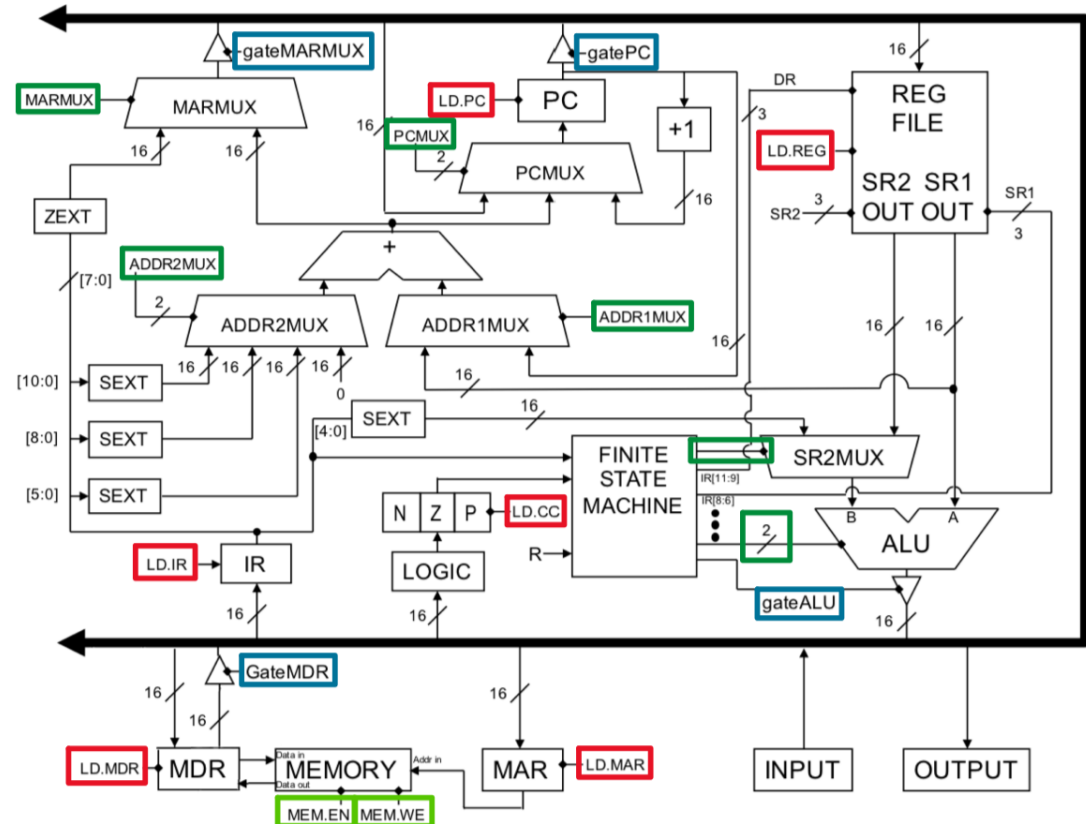- Used to move data around
 - LD.____** — write enable for a register
 - gate____** — tri-state buffer that allows data to go onto the bus
 - ____MUX** — selector for a multiplexer



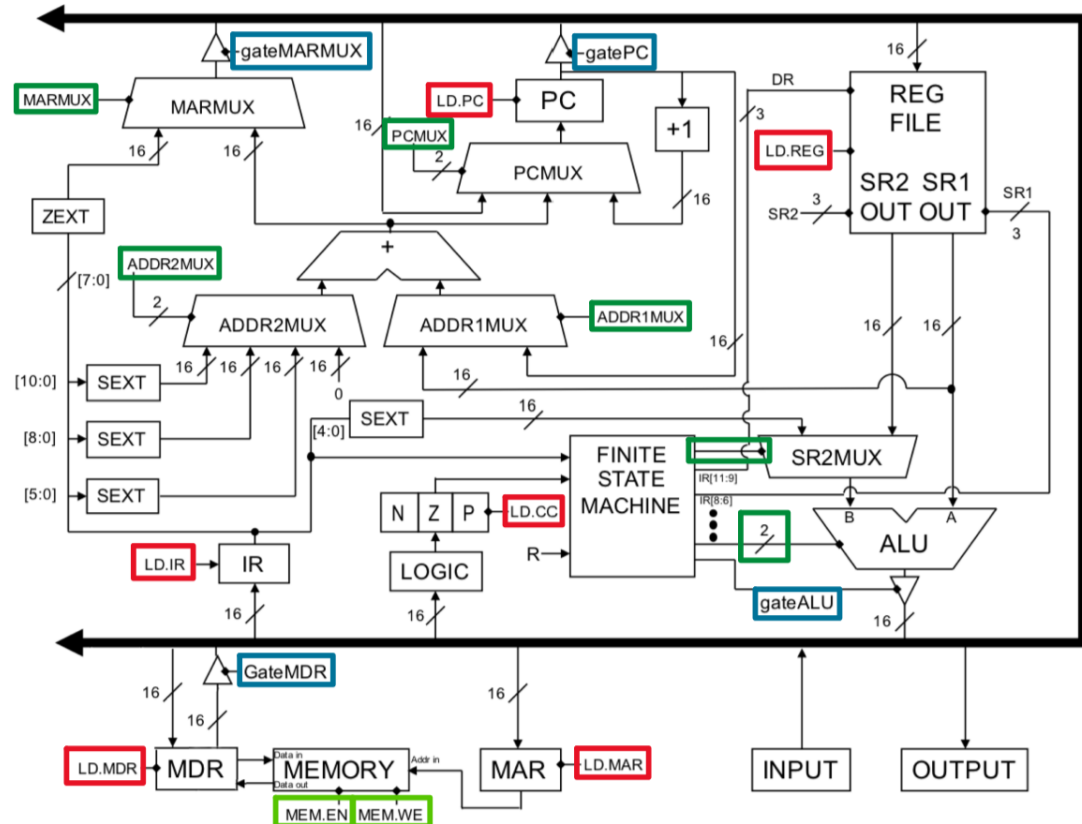Example

- Say we want to put the data from the PC (a register) into the MAR (another register). What signals do we turn on?



What is Memory? - Registers VS. Memory (RAM)



You have been exposed to **sequential logic**. (i.e. registers)

Registers: Used for quick data storage on the processor.

Random Access Memory:

- Memory is like a really big array
- Contains instructions for programs that are currently being executed.
- Stores any data a program may need.

The two “sides” of memory:

- Address side
- Data side (or Data @ Address)

NOTE: Everything here is technically in binary.

Memory Layout Example

This example is used to show the type of data that can be found in memory.



Addresses

Data @ Addresses

| | |
|--------|--------------------|
| 0x3000 | ADD R1, R2, R0 |
| 0x3001 | HALT |
| 0x3002 | 0b0010000100010000 |
| 0x3003 | 0x2110 |
| ... | ... |
| 0x300A | #8464 |


LC-3 Instructions:
Piece of some
program in memory.

Random Data in Memory:
Data used by a program
currently being executed.
OR
Left over data from an old
program previously executed.

Loading from Memory

Load data from memory:

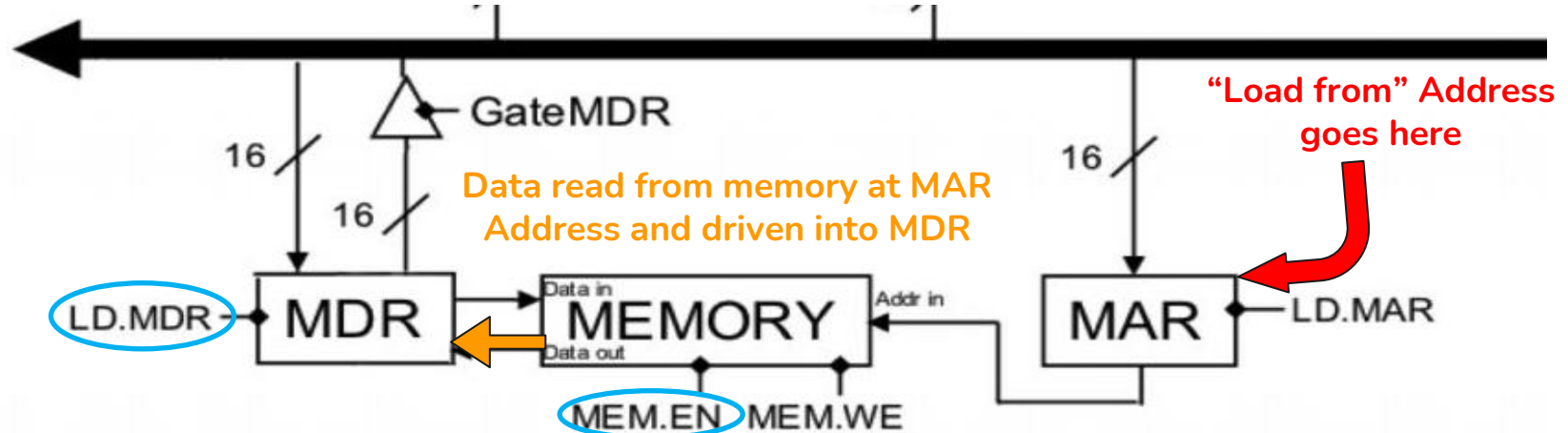
- Place the **address** of where the data is located in **MAR** (Memory Address Register).
- Memory is **read** from that address and “driven” to the **MDR** (Memory Data Register). After that, the data moves to its destination register.



Storing into Memory

Store data into memory:

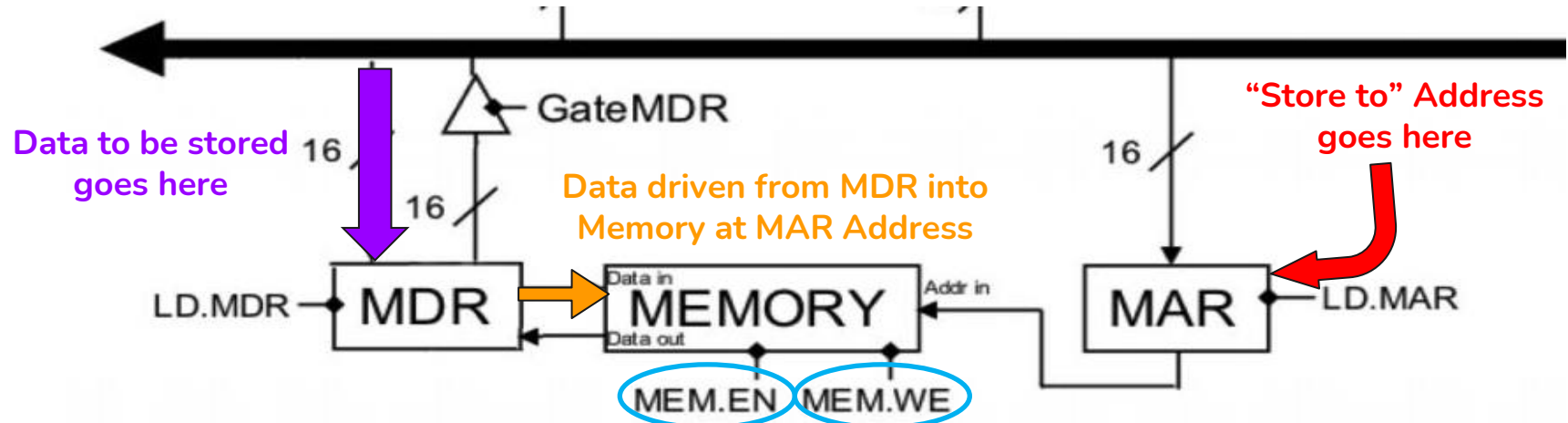- Data from a register is placed into the **MDR**.
- Address of where to store data is placed into the **MAR**.
- Data is stored in memory at the address specified by the **MAR**.







Note

- Every piece of data in memory is just 16 bits of binary
- How does the LC-3 know...
 - Which addresses contain data that's an instruction?
 - Which addresses contain data that's an integer?
 - Which addresses contain data that's a character?
- Answer: it doesn't!


ALU

- Two inputs:
 - SR1: Data from register
 - SR2: Data from register **OR** immediate value from the instruction
- Select bits come from Finite State Machine
 - 00 $\rightarrow A + B$
 - 01 $\rightarrow A \text{ AND } B$
 - 10 $\rightarrow \text{NOT } A$
 - 11 $\rightarrow \text{PASS } A \text{ (unchanged)}$
- Drives output onto bus
- Condition codes (CC)
 - Set when writing to general purpose registers, LD.CC flag
 - Only three possible states: 001, 010, 100
 - What do they each mean?

  


PC

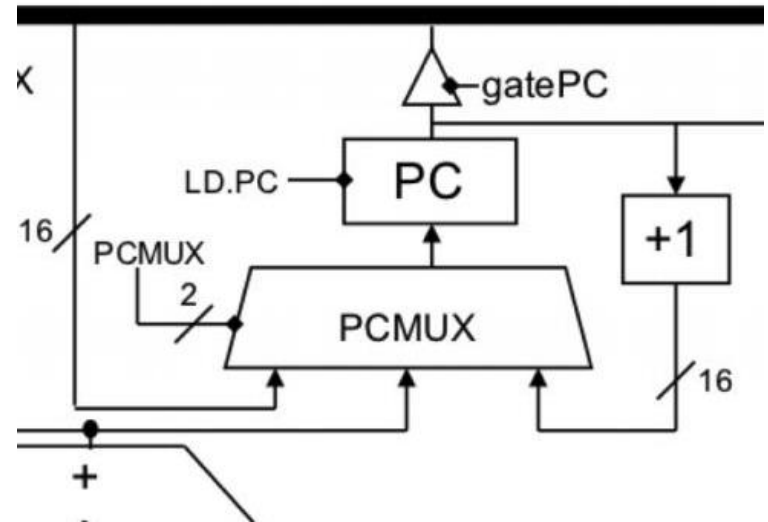- Holds the current program counter – address of next instruction to execute
- Repeat that: "the address of the *next* instruction to execute"
- It does NOT hold:
 - The current instruction
 - The address of the current instruction
- Three ways to update PC
 - PC + offset
 - PC + 1
 - Given a value for the PC via the bus
- The "correct" way is selected through PCMux




IR

 - Instruction register – holds the **value** of the **current** instruction
- For example, the instruction ADD R3, R1, R2 may look like:



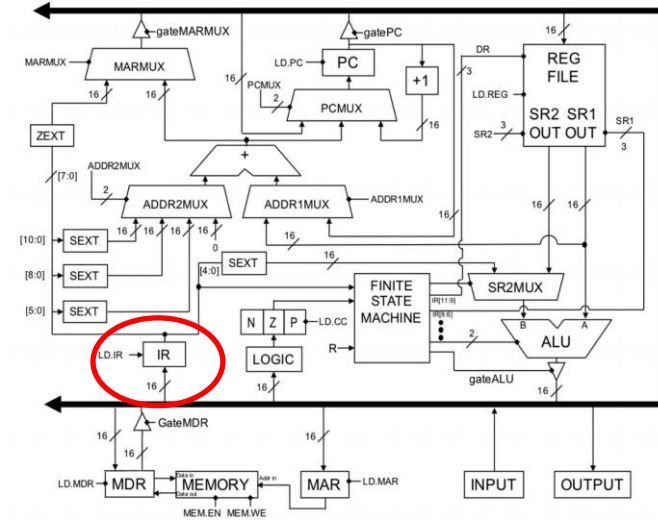- Having the correct value in the IR helps the FSM determine the current state and send the correct control signals
- A new value can be read from the bus (with signal LD.IR) and the current value is directly connected to relevant components




LC3 Instruction Set

| | | | | | | |
|-----|------|----|-----|---|-----------|-----|
| ADD | 0001 | DR | SR1 | 0 | 00 | SR2 |
| ADD | 0001 | DR | SR1 | 1 | imm5 | |
| AND | 0101 | DR | SR1 | 0 | 00 | SR2 |
| AND | 0101 | DR | SR1 | 1 | imm5 | |
| BR | 0000 | n | z | p | PCOffset9 | |

| | | | | | | |
|-----|------|----|-----------|---------|--|--|
| LD | 0010 | DR | PCOffset9 | | | |
| LDI | 1010 | DR | PCOffset9 | | | |
| LDR | 0110 | DR | BaseR | offset6 | | |
| LEA | 1110 | DR | PCOffset9 | | | |
| NOT | 1001 | DR | SR | 111111 | | |
| ST | 0011 | SR | PCOffset9 | | | |
| STI | 1011 | SR | PCOffset9 | | | |
| STR | 0111 | SR | BaseR | offset6 | | |

Executing Instructions

 

Instruction execution has three "stages", called *macrostates*


- Each macrostate is made of one or more *microstates* (1 per clock cycle)
- The microstates are the states in the microcontroller's state machine!

The macrostates are:


1. Fetch (3 clock cycles)
 - Load the next instruction from memory into the instruction register (IR)
 - Increment the PC
2. Decode (1 clock cycle)
 - The microcontroller looks at the instruction to figure out how to execute it
3. Execute (varies)
 - The microcontroller steps through several microstates and asserts the correct control signals to execute the instruction

The book splits up executing instructions into seven phases. This is a more conceptual overview of how it works and is unrelated to the three macrostates.


Fetch: Part 1

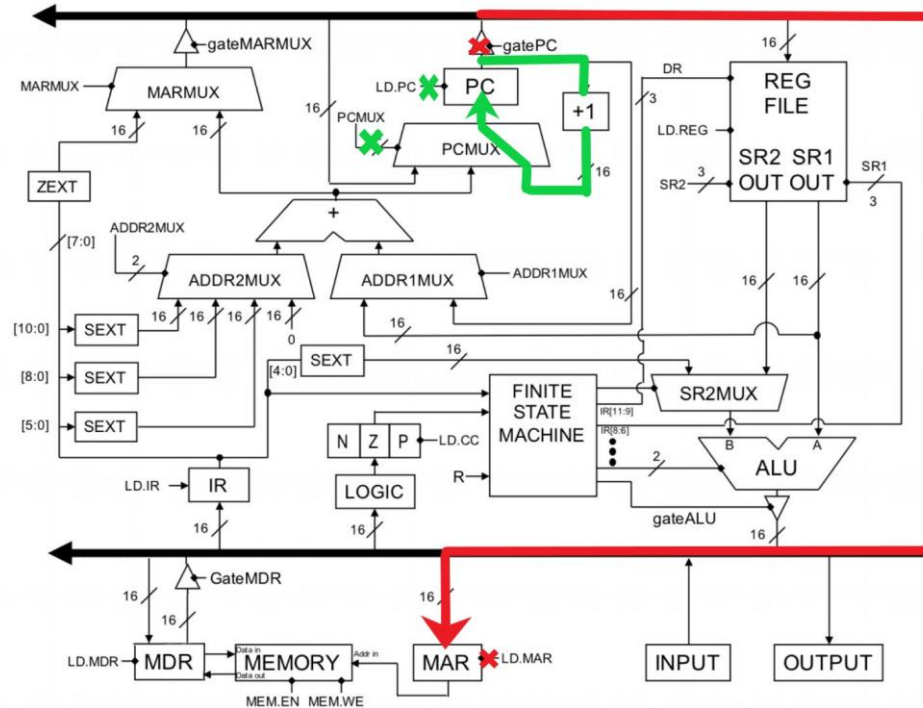


Fetch: Part 2

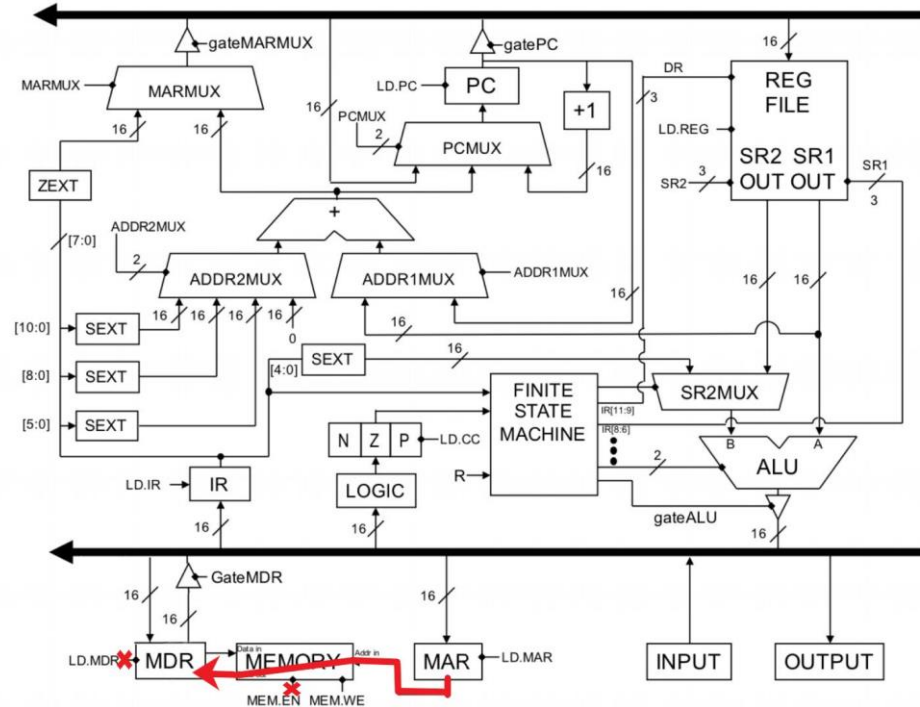


Fetch: Part 3

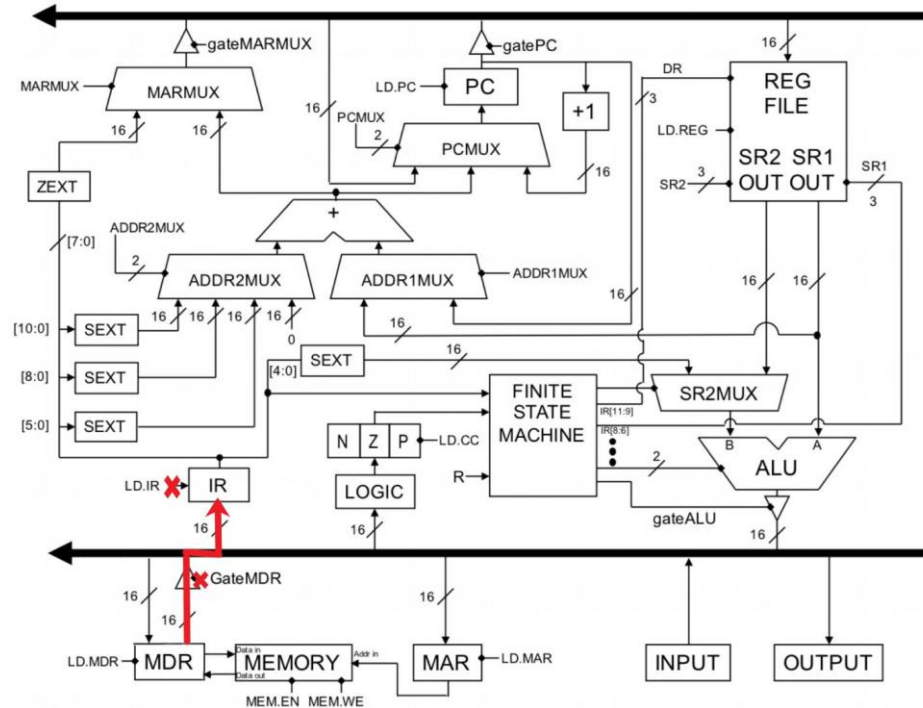


What is MEM.EN used for?

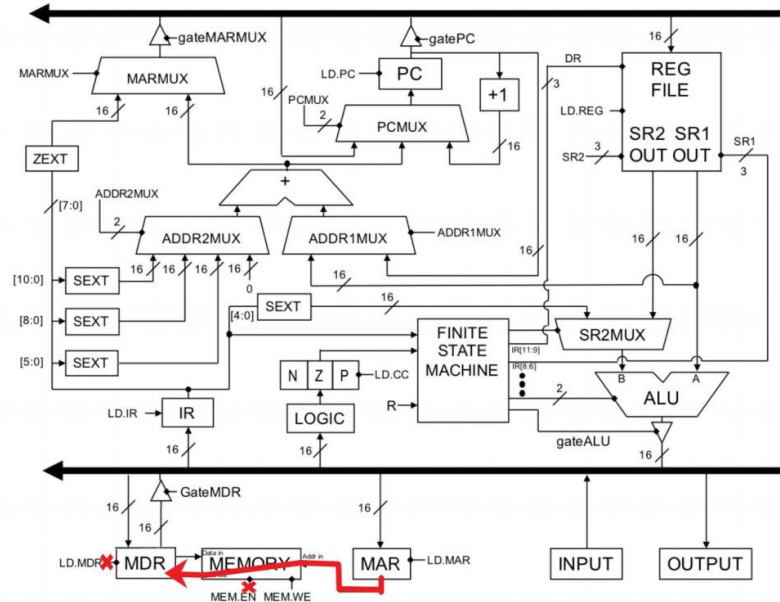


Execute: immediate ADD

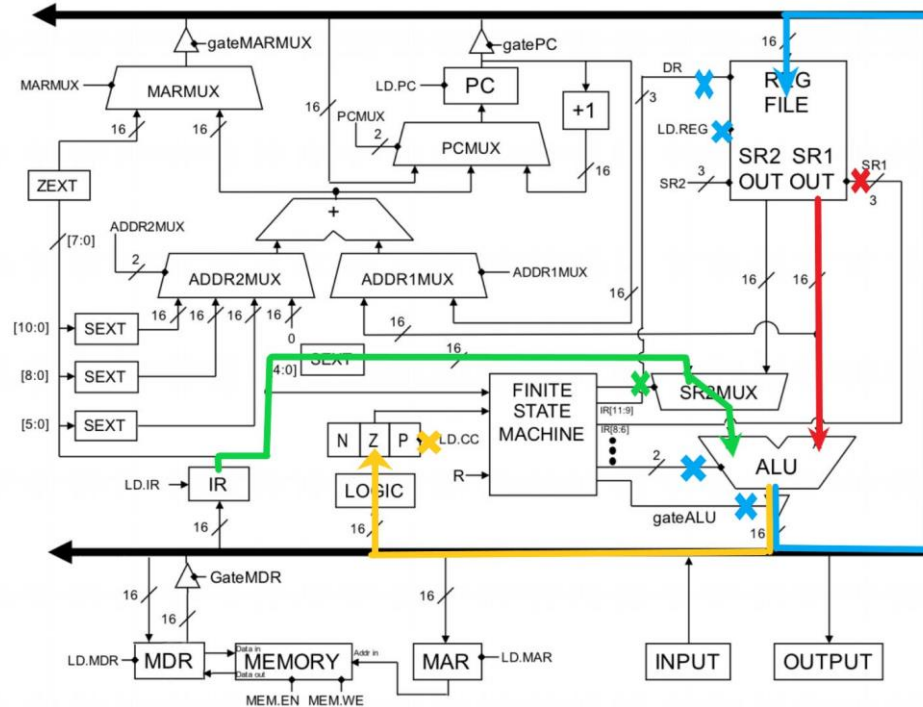


Why do we need the SR2MUX?

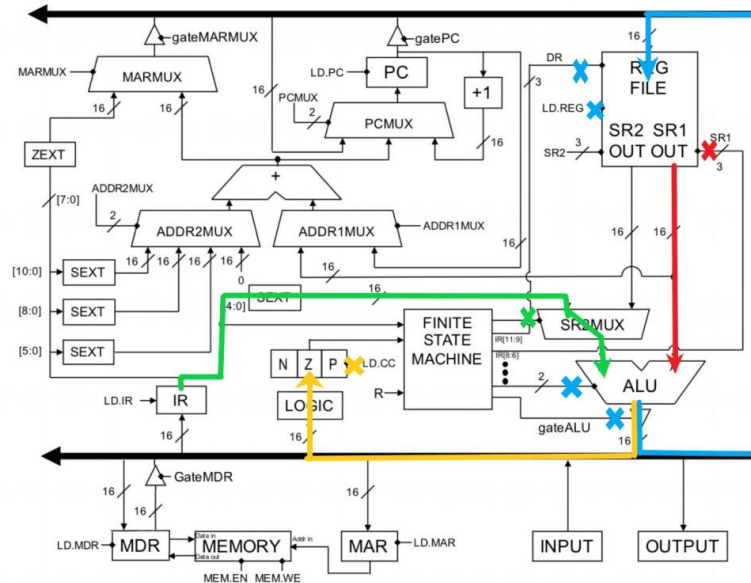


Execute: STR (Part 1)

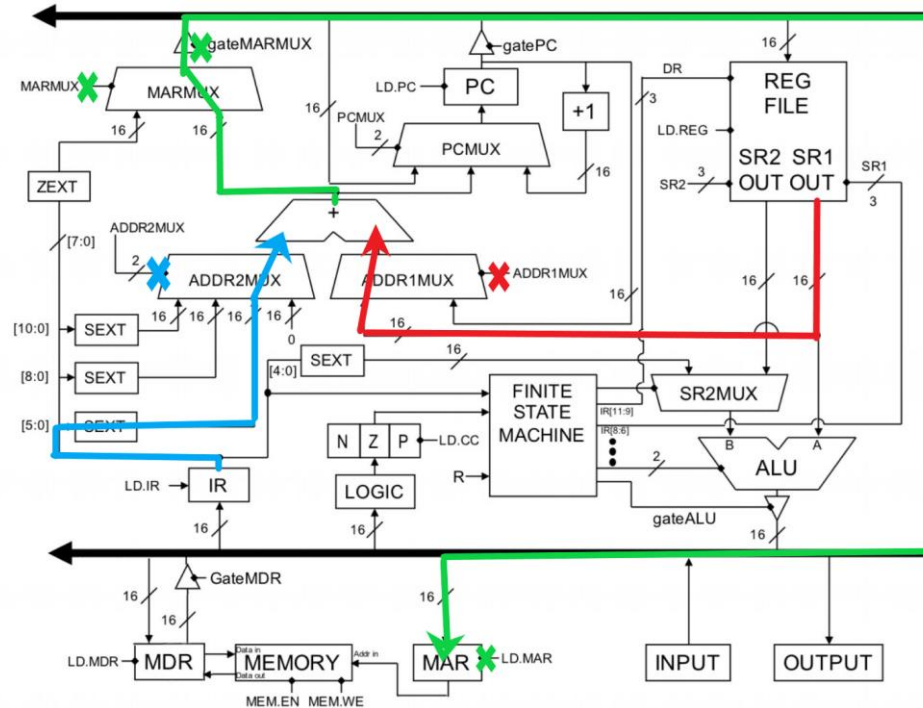


Execute: STR (Part 2)

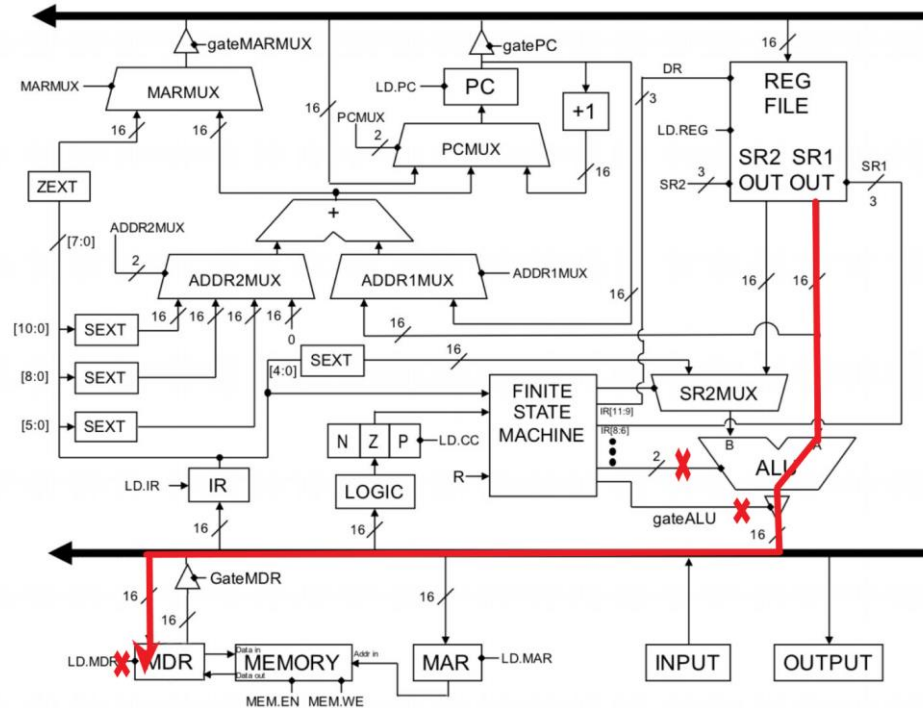

Execute: STR (Part 3)

 


LC-3 Execution Cycle

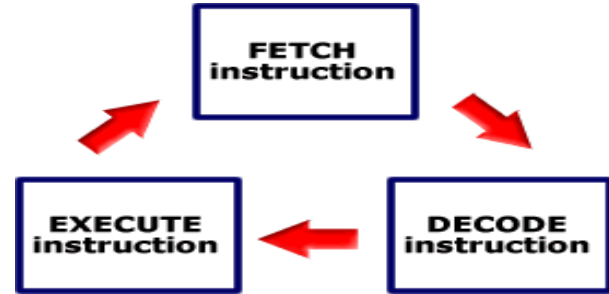

- The LC-3 cycles between three *macrostates*:
 - **Fetch** (obtaining the instruction at the address stored in the PC)
 - **Decode** (determining which instruction to execute by reading the opcode)
 - **Execute** (doing whatever the instruction says to do)
- The current macrostate is tracked inside the FSM. Some take multiple clock cycles to execute.

DECODE

 - Now that the IR contains the instruction, the FSM can read the opcode.
- If the instruction is BR (branch), the FSM will also check the condition codes to ensure that the branching condition is met.
- The FSM will change to a specific state depending on the opcode. This takes a clock cycle in the LC-3, but some computers can combine DECODE with the last cycle of FETCH.





EXECUTE

- Once the instruction is decoded, the EXECUTE macrostate begins.
- Each instruction causes the EXECUTE phase to act differently.
- The EXECUTE macrostate takes a variable number of clock cycles; some instructions like ADD are quick, while others like LDI take longer.
- Once the EXECUTE macrostate completes, the FETCH macrostate restarts, using a new PC address—generally, this is the next instruction in memory
- You will be implementing the EXECUTE macrostate for many instructions (as well as the FETCH macrostate) in HW4

LC3 Instruction Set

| | | | | | | |
|-----|------|----|-----|---|-----------|-----|
| ADD | 0001 | DR | SR1 | 0 | 00 | SR2 |
| ADD | 0001 | DR | SR1 | 1 | imm5 | |
| AND | 0101 | DR | SR1 | 0 | 00 | SR2 |
| AND | 0101 | DR | SR1 | 1 | imm5 | |
| BR | 0000 | n | z | p | PCOffset9 | |

| | | | | | | |
|-----|------|----|-----------|---------|--|--|
| LD | 0010 | DR | PCOffset9 | | | |
| LDI | 1010 | DR | PCOffset9 | | | |
| LDR | 0110 | DR | BaseR | offset6 | | |
| LEA | 1110 | DR | PCOffset9 | | | |
| NOT | 1001 | DR | SR | 111111 | | |
| ST | 0011 | SR | PCOffset9 | | | |
| STI | 1011 | SR | PCOffset9 | | | |
| STR | 0111 | SR | BaseR | offset6 | | |